

# Electronic Hardware

Onboarding: 555 Timer Explanation

#002




# Introduction

## Agenda:

1. Intro to LM555
2. Intro to N-Channel MOSFET
3. Putting Everything Together
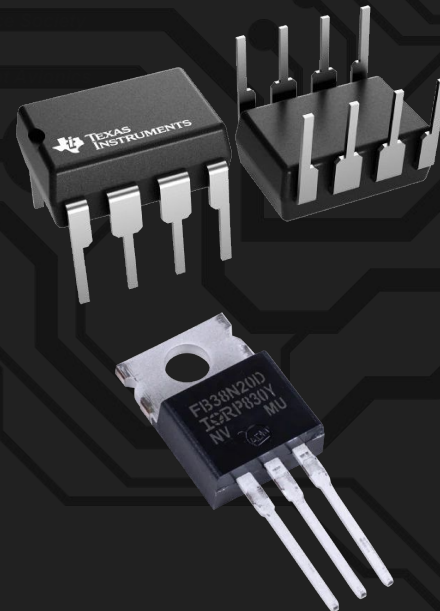
## Goal:

Understand the expected behavior of the 555 Timer Circuit



## What is it?

- A square-wave generator controlled by using different resistors and capacitors

## How to Use It?

- Two modes: **Astable** (our application) and Monostable
  - Astable Operation: Its state is Astable (not stable), and it will generate a consistent square wave
- Application:
  - Follow the diagram shown on the right
  - Use the formula given to calculate the frequency and duty cycle based on resistance and capacitance (**note that the duty cycle formula gives us % time output is low**)
- But How Does It Work?:
  - A great explanation video by Ben Eater: [Astable 555 Timer - 8-bit computer clock - part 1](#)

### 7.4.2 Astable Operation

If the circuit is connected as shown in Figure 14 (pins 2 and 6 connected) it will trigger itself and free run as a multivibrator. The external capacitor charges through  $R_A + R_B$  and discharges through  $R_B$ . Thus the duty cycle may be precisely set by the ratio of these two resistors.

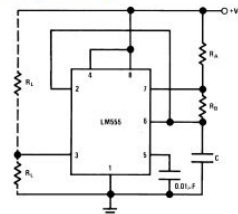


Figure 14. Astable

In this mode of operation, the capacitor charges and discharges between  $1/3 V_{CC}$  and  $2/3 V_{CC}$ . As in the triggered mode, the charge and discharge times, and therefore the frequency are independent of the supply voltage.

Figure 15 shows the waveforms generated in this mode of operation.

The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C \quad (1)$$

And the discharge time (output low) by:

$$t_2 = 0.693 (R_B) C \quad (2)$$

Thus the total period is:

$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C \quad (3)$$

The frequency of oscillation is:

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B) C} \quad (4)$$

Figure 16 may be used for quick determination of these RC values.

The duty cycle is:

$$D = \frac{R_B}{R_A + 2R_B} \quad (5)$$




# Intro to N-Channel MOSFET

## What is it?

- N-Channel Metal-Oxide-Semiconductor Field-Effect Transistor
- We are using it as a voltage-controlled switch
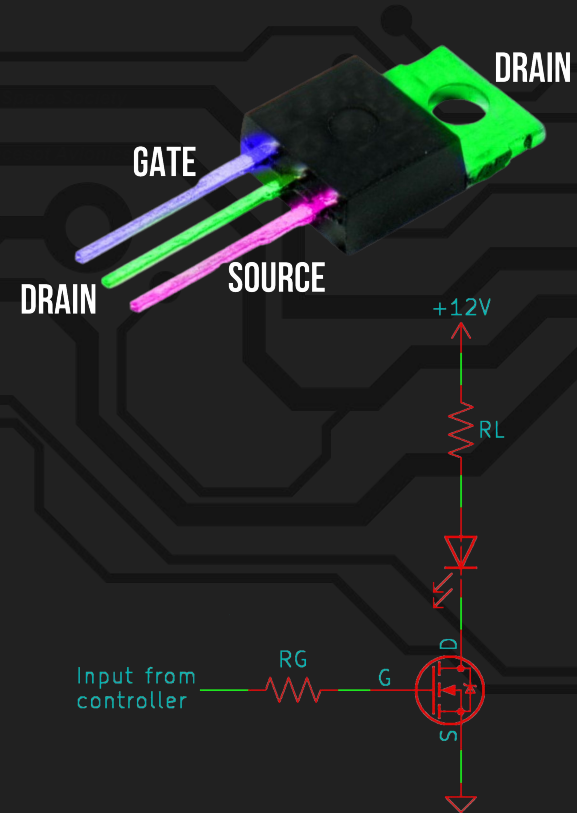
## How to Use it?

- Off when no voltage applied to Gate pin
  - Very large resistance between Drain and Source
  - Only a few **Micro Amp** can go through
- When a voltage is applied to Gate pin
  - When the voltage difference between Gate and Source ( $V_{GS}$ , which is  $V_{Gate} - V_{Source}$ ) is larger than the Threshold Voltage ( $V_{TH}$ ,  $\sim 2.5V$  in our case), it turns on
  - The resistance between Drain and Source reduce based on the difference between  $V_{GS}$  and  $V_{TH}$
- Source pin usually connected to GND when using N-Channel



# Putting Everything Together

## Our Application

- 555 Timer generates 9V square waves to drive the MOSFET
- MOSFET turns on and off to blink the LEDs


## Calculations

- MOSFET:
  - Because  $V_{GS}$  has to be larger than  $V_{TH}$  (~2.5V) and we know  $V_{Gate}$  is 9V, so  $V_{Source}$  will be ~6.5V
- 555 Timer:
  - $R_A = R_B = 50K\text{ Ohm}$ ,  $C = 10\text{ uF}$

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B)C} = \frac{1.44}{(50 \times 10^3 \text{ Ohm} + 2 \times 50 \times 10^3 \text{ Ohm}) 10 \times 10^{-6} \text{ F}} = 0.96 \text{ s}$$

$$D = \frac{R_B}{R_A + 2R_B} = \frac{50 \times 10^3 \text{ Ohm}}{50 \times 10^3 \text{ Ohm} + 2 \times 50 \times 10^3 \text{ Ohm}} = 0.33$$

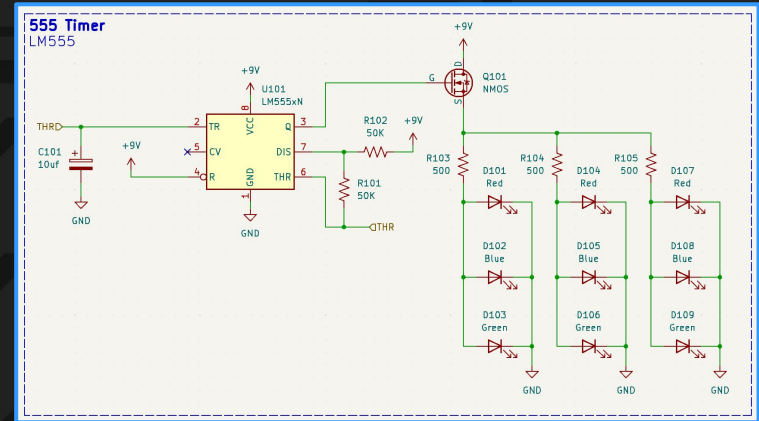- Remember that duty cycle gives % time output is low (0V)
- So % time output is high (9V) =  $1 - 0.33 = 0.67$



The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C \quad (1)$$

And the discharge time (output low) by:

$$t_2 = 0.693 (R_B) C \quad (2)$$

Thus the total period is:

$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C \quad (3)$$

The frequency of oscillation is:

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B) C} \quad (4)$$

Figure 16 may be used for quick determination of these RC values.

The duty cycle is:

$$D = \frac{R_B}{R_A + 2R_B} \quad (5)$$



# Further Reading

## Works Cited:

Ben Eater. "Astable 555 timer - 8-bit computer clock - part 1." *YouTube*, Mar. 2016, <https://www.youtube.com/watch?v=kRISFm519Bo>.

"FQP30N06L 60V LOGIC N-Channel MOSFET." *Fairchild Semiconductor*, May 2001, <https://cdn.sparkfun.com/datasheets/Components/General/FQP30N06L.pdf>.

"LM555 Timer Datasheet." *Texas Instruments*, Jan. 2015, [www.ti.com/lit/ds/symlink/lm555.pdf](http://www.ti.com/lit/ds/symlink/lm555.pdf).

## Image Source:

<https://www.mouser.com/new/infineon/infineon-200v-250v-hexfet-mosfets/>

<https://www.ti.com/product/LM555/part-details/LM555CN/NOPB>

<https://oscarliang.com/how-to-use-mosfet-beginner-tutorial/>