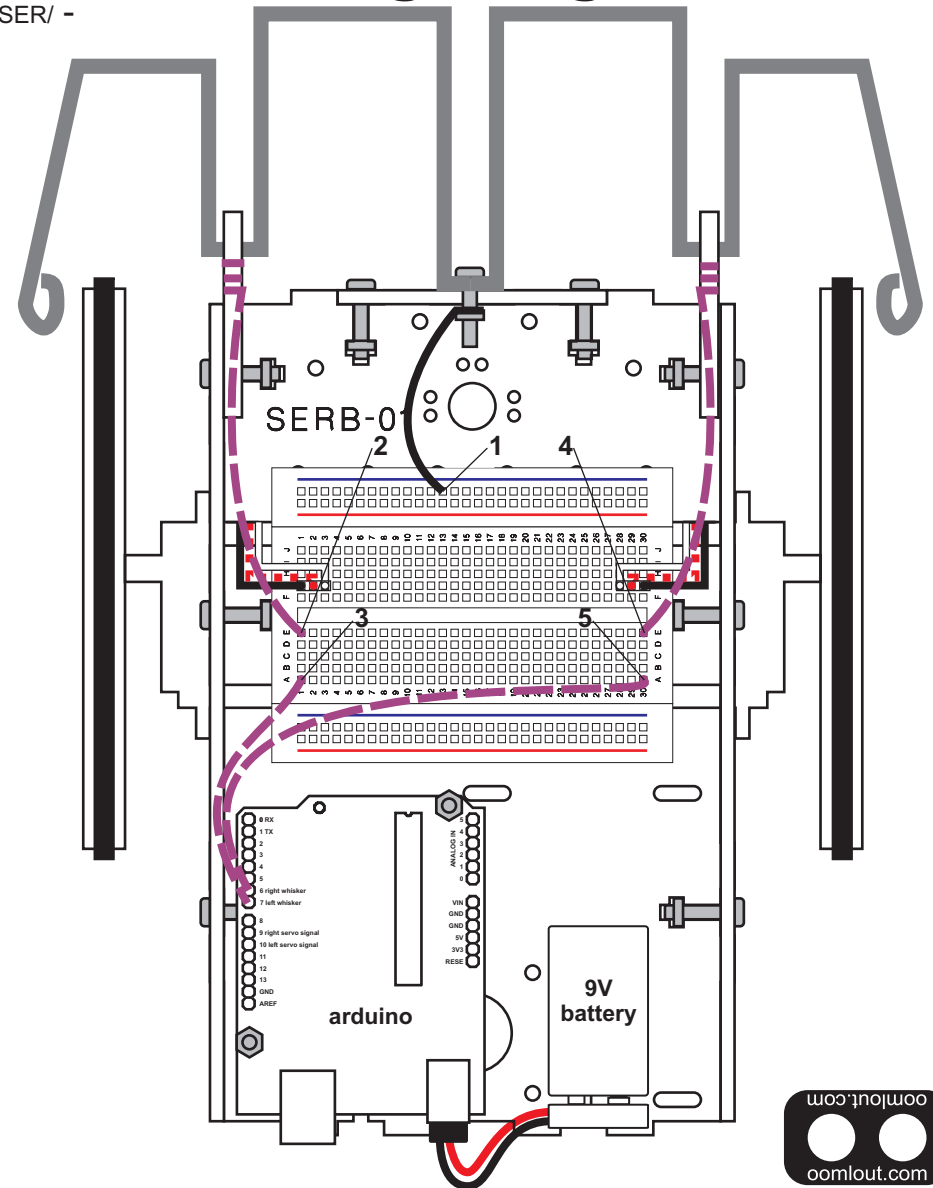






Arduino Controlled Servo Robot (SERB) - Whisker Wiring Details

- Wire up your Arduino Controlled Servo Robot (SERB)
- According to the wire details found here
- http://www.instructables.com/id/How_to_Make_an_Arduino_Controlled_Servo_Robot_SER/ -
- 1. whisker common to breadboard ground
- 2. left whisker to breadboard
- 3. left whisker breadboard to arduino (pin 7)
- 4. right whisker to breadboard
- 5. right whisker breadboard to arduino (pin 6)

Wiring Diagram



Colour Key

-  black
-  red
-  white
-  purple