

This document should be read alongside

# Schematic diagram. Note: - Schematics show a bare board, rather than it sitting in the breakout

# 'Build a Box' document. Details how to mark out, cut and mount everything into a project box.

It also has photos detailing the finished wiring.

All of the boards are pre-made, you will not have to solder the components yourself. Most boards will also have the header pins pre-soldered. The GY-302 (light-meter) and the LED matrix require the header pins soldered. Soldering is also required for the buttons, flash socket and external connectors, if you choose to use them.

JST HX cables are used to connect the different modules to the breakout board. They make a neat solution and fit tightly to the header pins on the modules, so do not work loose like Dupont wires.

There are many 3.3V, 5V & GND power connections. These will not all fit into the breakout board screw-terminals. It will be necessary to connect them in groups with a choc-block or similar, then take one wire to the screw terminal.

**Whilst it is not good practice to mix voltages, there is no way to avoid this, as some modules require 3.3V and others 5V. Please take care to ensure the correct voltage is supplied to each module and on the correct pin.**

Light-meter, LED matrix and LCD all require 5V. If not using these modules, then 5V wiring is not required.

**Ensure you pay particular attention to the polarity of the connections. The boards are clearly marked.**

**The LCD** is marked Vcc and is connected to 5V. (Red wire) and GND, (Black wire)

**The GY-302 Light Sensor** is marked Vcc and is connected to 5V (Red wire) and GND, (Black wire)

**The Laser tx board** is marked as S (3.3V) and - (GND) Do not connect anything to the centre pin.

On many Laser boards, the Laser barrel is only held to the board by its wires. This means it can easily be knocked out of alignment. Consider using hot-glue or similar to affix the Laser barrel to the board.

**The Sensor (rx) board** is marked VCC (3.3V) and GND. The centre pin is marked OUT, which is wired to one of the input pins on the ESP32 breakout board.

Be very careful when fitting the receiver sensor into the board. Refer to the photograph. The little lens must be pointing towards the header pins on the board.

**The TFT** is marked VDD (3.3V) and GND (0V). The TFT board LED pin is also connected to 3.3V

It is recommended that The Shutter Tester is built with the TFT screen. However, it can be omitted, as all results are also sent to the computer screen.

## JST HX connectors.

*Using the kit containing separate plastic shells and pre-made wires is the easiest option. The wires can then be assembled in the correct colour order.*

*Note: - The kit does not include Brown & orange wires, or an 8-way connector. Either purchase the additional colours (details in the parts document) or substitute for different colours.*

*Similarly, either buy a separate 8-way connector or carefully cut the top lip from a 7-way and 2-way connector, so they will fit (only using one pin in the 2-way connector)*


JST HX cables can also be purchased pre-assembled. These were used for the prototype and shown in the photos. However, the pins require removal to be re-ordered to the correct colour sequence, which is quite fiddly.

The wires are quite thin, so good quality wire strippers designed for fine wiring are required. Alternately a sharp Stanley knife or scalpel can be used to carefully remove the insulation. Tinning the bare wire (adding a little solder to it with a soldering iron) helps it gain thickness, to better be gripped in the screw terminals.

If using the pre-made assemblies,

To keep the colour coding correct, some pins on the JST HX connectors will require removing and swapping.

To do this, carefully press down on the exposed side of the metal pin, to push the barb down and then slide the pin & wire out of the connector. It does take a little practice and if too much force is used, the barb can be pushed down too far making it impossible to bend back up, for re-inserting. It is worth sacrificing one connector to practice on, to get the hang of doing it. If all else fails, the pins can be re-inserted without the barb and a dab of-hot-glue used to hold the wire in the plastic connector.

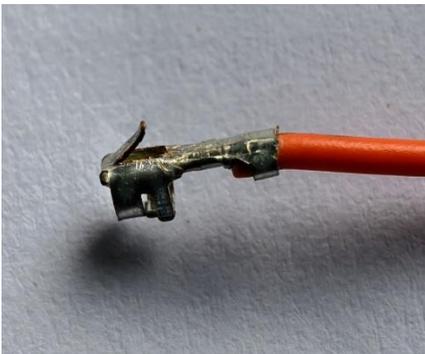


This is the connector removed from the plastic housing. The barb can be seen protruding at the top.

During removal, the barb was pushed too far down, taking a lot of effort with a sharp thin blade, whilst wearing protective gloves and keeping the knife pointing away, to get the barb bent back up, as is evident by all the scratch marks



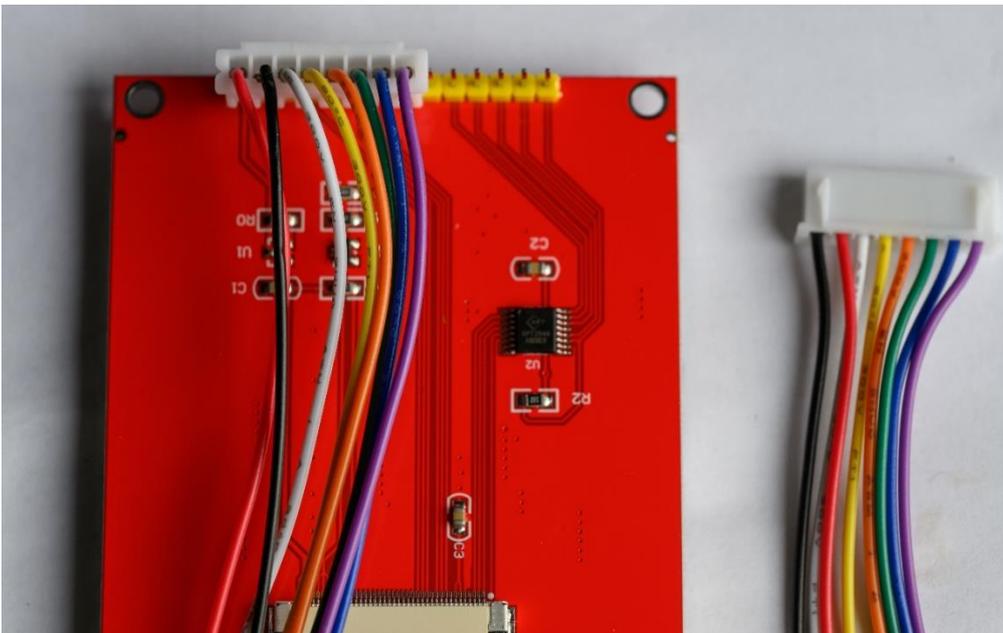This is the encoder, showing the required changes to the pre-assembled JST HX connector. On the right, the original connector and on the left, Red has been moved to the left and Black to the right, with orange being placed in the second position (vacated by the Red)



The JST HX connector, 8-pin. Red & Black require swapping. Original connector shown on the right. The unused pins on the tft board are for touch, which is not implemented in the Shutter tester and are left disconnected.



Wiring for the TFT screen, encoder and buttons.

Orange terminal connectors have been glued to the board using epoxy resin.


Top terminal connectors are +3.3V and 0V

Bottom terminal connectors are not yet connected, but will be 0V and +5V
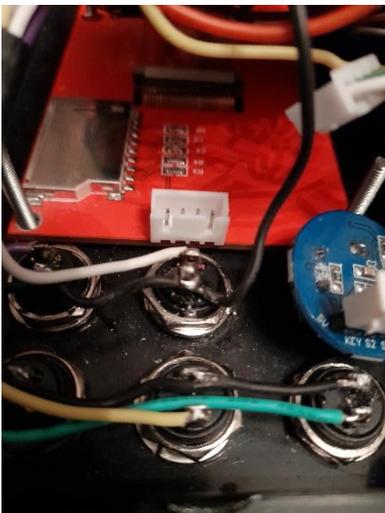
### **SD card connections.**

The SD card slot on the TFT board can be used for data logging if required. SD card must be formatted FAT32 and be no larger than 32Gb

The board does not have a connector fitted, so a 4-way JST HX socket was soldered onto the board and a slot cut into the project box for insertion of the SD card.



## LCD.

The LCD is a legacy from the Arduino unit and cannot display as much information as the TFT or PC screen. The LCD is depreciated and may not be supported in future firmware updates.

In place of the LCD, a larger font and simplified display has been added to the existing TFT screen, allowing the user the option of detailed or larger simplified display.

**Note:** - The specified project box is too small to house the LCD.

## Flash connections.

The flash connection can be used to detail when the flash will fire during the shutter cycle, to ensure it is triggered at the correct time. A suitable cable and 3.5mm socket is detailed in the parts document. Two wires require soldering to the socket.

**Note:** - only cameras with mechanical flash contacts should be connected.




Connections to 3.5MM jack socket.

## Button Wiring.

A black wire is connected to one leg on each button in a daisy-chain and then run to the 0V connector block. The other leg on each button is connected to the corresponding screw terminal on the breakout board.

The wires used were the same colour as the buttons, except for the Black button, where a grey wire was used and the red button, where a purple wire was used.

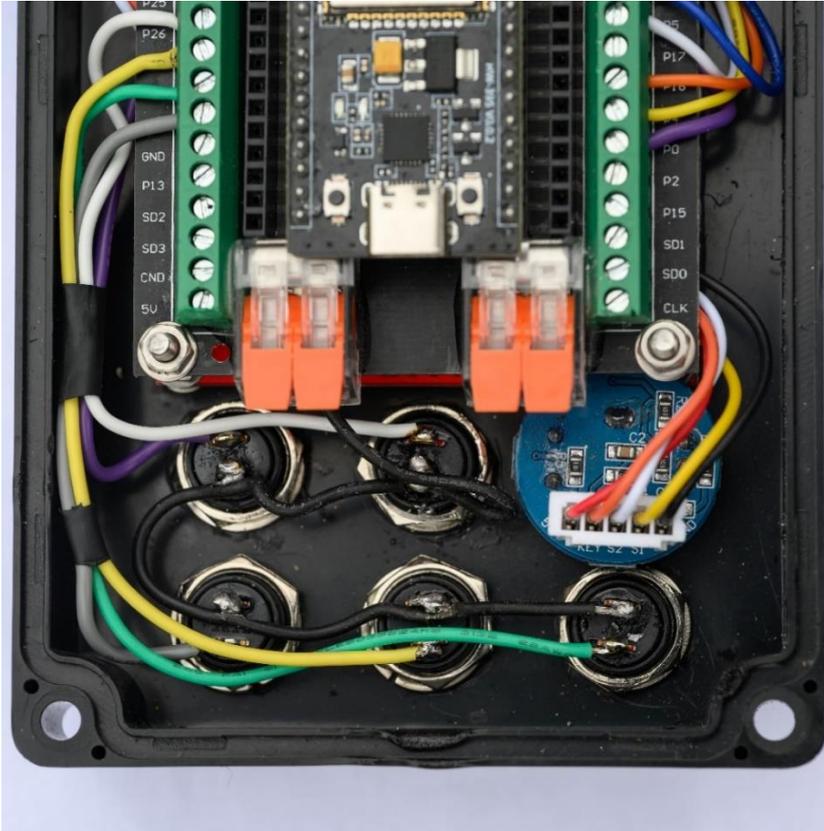A single colour wire can be used for all the buttons, but avoid using Red or Black.



Close up of button wiring. Black wire is common to all buttons and then goes to 0V. Grey wire has been used for the Black button and a purple wire for the Red button to avoid confusion with +V and 0V wires.

## Other Module wiring

LED matrix and light-meter can be connected using JST HX connectors. The wires will require extending.

An alternate is to purchase JST HX bare pin connectors (female type) and a crimp tool, to attach them to the end of the multicore cable. Suitable connectors & crimp tools are available on AliExpress. Or solder the wires directly to the module.

The multicore cable can be run directly into the project box and to the corresponding terminals on the breakout board. An alternate is to use a plug & socket mounted on the project box.


**Extreme care** must be used if using plugs & sockets, that dedicated pins are used for 3.3V and 5V. Connecting voltage to a data pin of a module is likely to destroy it.



Wiring for the Light-meter.

+5V is on the bottom right pin and 0V the bottom large flat pin  
Going anti-clockwise, the next pin is not used, the next pin is Yellow.  
The centre pin is White.

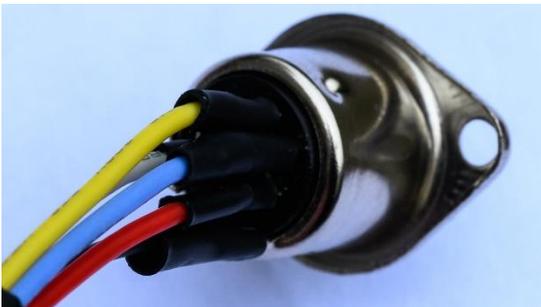Additionally, the bottom left pin (unused here) has been insulated as it is used for 3V for other sensors.



The LED matrix uses +5V (Bottom right) 0V bottom flat pin  
and anti-clockwise, the next two pins for Blue and Yellow.  
Centre pin is White

All pins have been insulated with shrink tube, to ensure no short can occur.

Additionally, the bottom left pin (unused here) has been insulated as it is used for 3V for other sensors.

## Sensors & Laser wiring.

All of the 3.3V connections, marked as 'S' on the Laser board and 'Vcc' on the sensor board can be linked together in a daisy chain. Then the same with the 0V connections.

Alternately JST HX connectors can be used on each of the boards (pins will require swapping to ensure power colour codes are followed) and the ends of these joined together.

The centre pin on each of the sensor boards has its own wire going back to the ESP32 breakout board.

The multicore cable can be run directly to the breakout board, or a plug & socket used on the exterior of the project box. Using a plug & socket will allow the sensor frame to be changed, for example from a horizontal to a vertical layout.

If using a plug & socket, an 8-pin version would allow two modules (sensors/Lasers & light meter for example) to both use an 8-pin connector to save money, as they come in packs of 5.

Be very careful with the 3V and 5V wires, ensuring they do not come into contact with any of the data pins.



8 pin Din socket wiring. 0V is the large flat terminal at the bottom.  
Red is 3V and used the bottom left pin.

The pins are very tightly spaced, so the +3V and 0V have been insulated with shrink tube to avoid any short circuits. Blue, Green, Yellow then use the next three pins, going clockwise.

Additionally, the bottom right pin (unused here) has been insulated as it is used for 5V for other modules.

*A safer alternate is to use different styles or pin configurations for each of the connectors.*

*For example purchase*

*8-pin connectors for the sensor board,*

*5-pin for the Light-Meter.*

*6-pin for the LED Matrix (this device is more of a curiosity & most people do not include it)*

*3.5mm jack socket for the flash.*






For the prototype, to make the sensor unit, two pieces of wood were cut, one 40mm high, to mount the Lasers (tx). The other 28mm high, to mount the sensors (receivers, rx) Spacers under the camera (scrap wood, beer mats etc) used to raise different camera models to the correct height.

The Laser & sensor modules were hot-glued to the top of the wood. Hot-glue allows the lasers to be moved for alignment, whilst the glue cools.

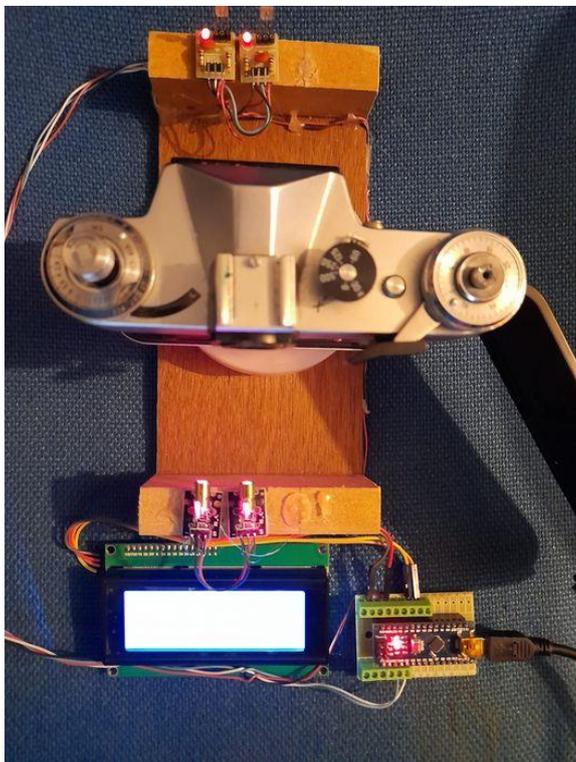
The below photo shows the Arduino prototype, which used two sensors and Lasers.



Prototype shutter tester with two Lasers.

In this example, wires (taken from an Ethernet cable) are directly soldered to the Laser boards, rather than jumper wires being used.

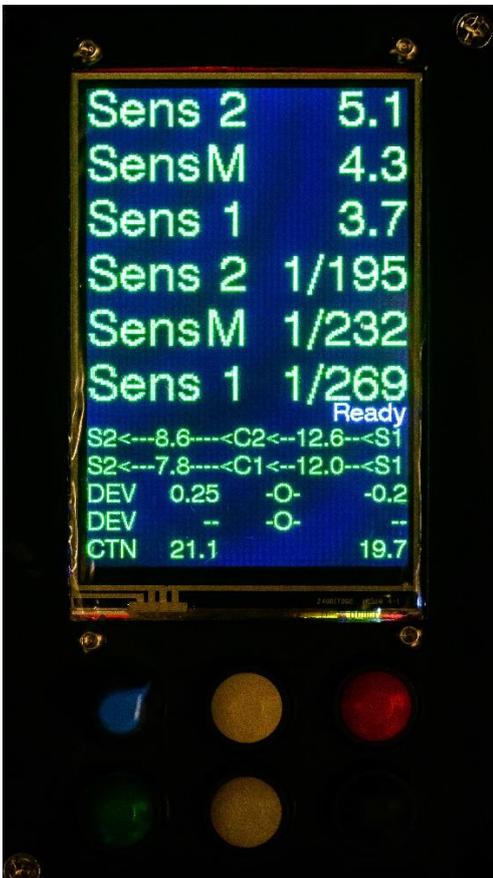This simple design works perfectly well & the third Laser & sensor for the ESP32 version easily added.



Here is the 158-90-60 project box with just the TFT display.  
 (It is displaying the Simple Screen, which has been added to replace the LCD).



Here is the ESP32 Shutter Tester in a larger 200-120-75 project box, with both TFT & LCD. The LCD is mounted in an acrylic frame and bolted to the top of the project box.






Compact version in 3d printed case




Inside the compact version.

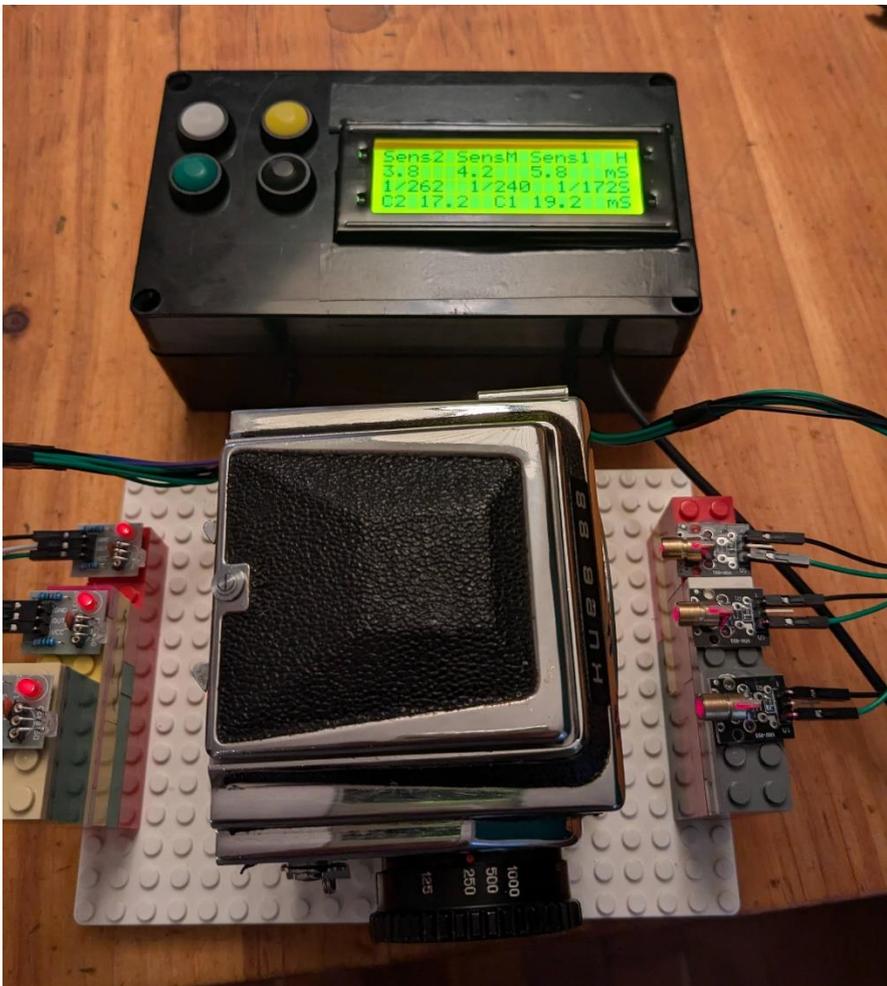

Lego version, testing a medium format camera.



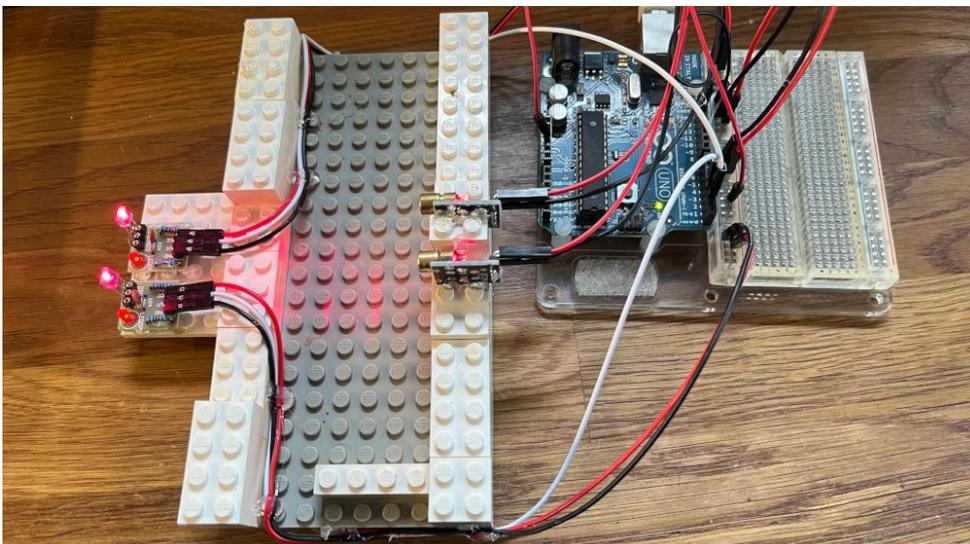3d printed version. Note lasers & sensors are arranged diagonally, 32mm spacing horizontally & 20mm vertically. This way the same sensor frame can be used for horizontal or vertical shutters. It does however make it a little more tricky to line up the film-gate with the Lasers.




Lego :o)




Horizontal or vertical shutters. Switch toggles horizontal or vertical Lasers.



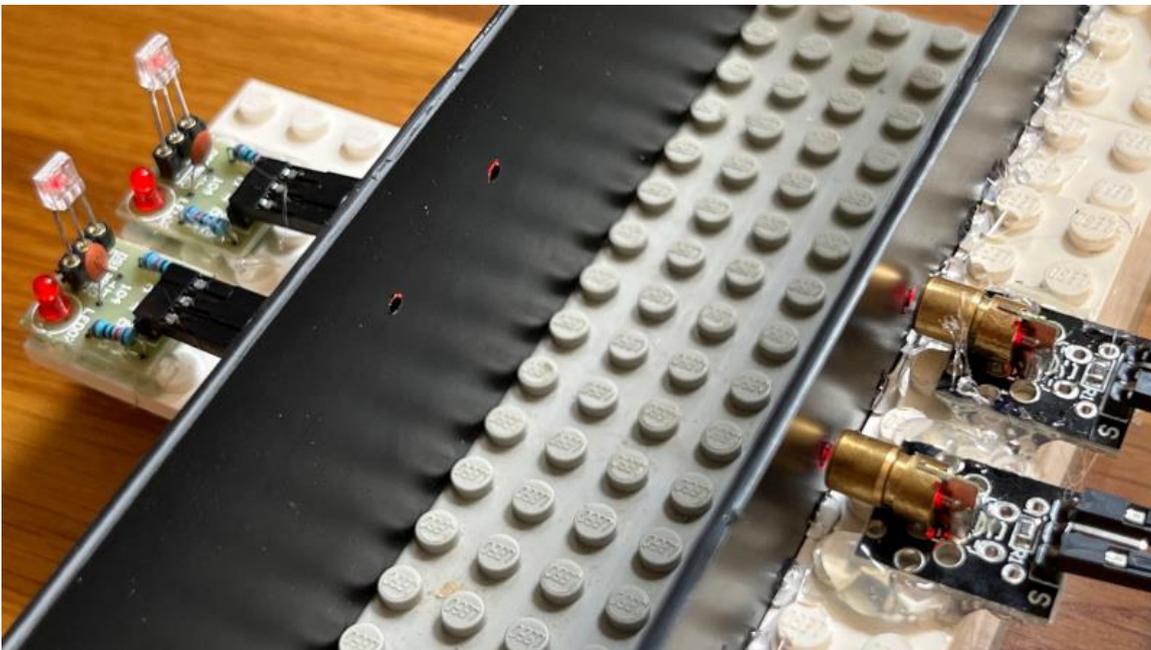Chopping board used for base and electrical socket boxes used to house sensors & Lasers.



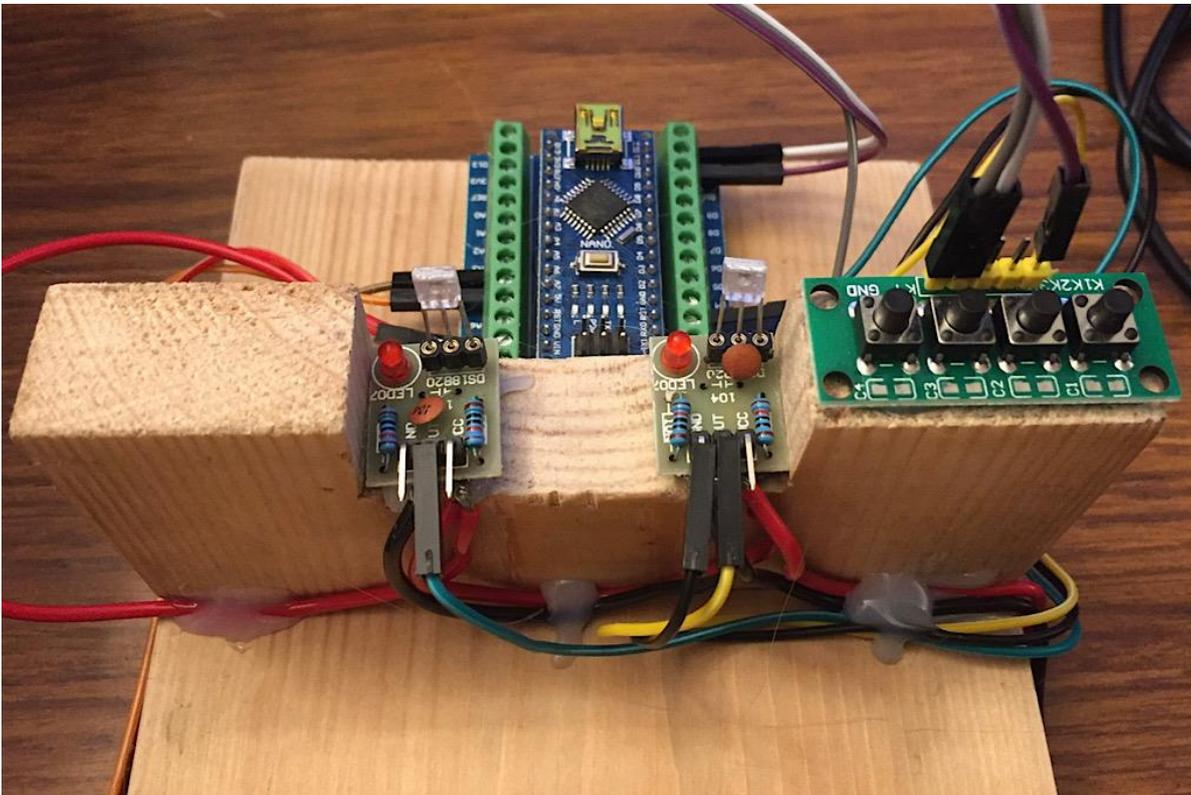Mask added to the Lego version, for better accuracy at higher shutter speeds.



Simple 'block of wood' sensor frame.

