

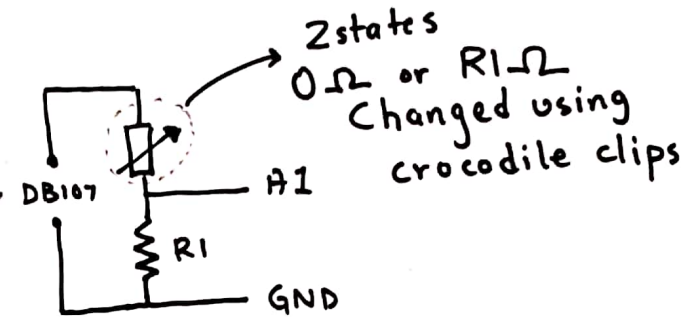


# Voltmeter circuit

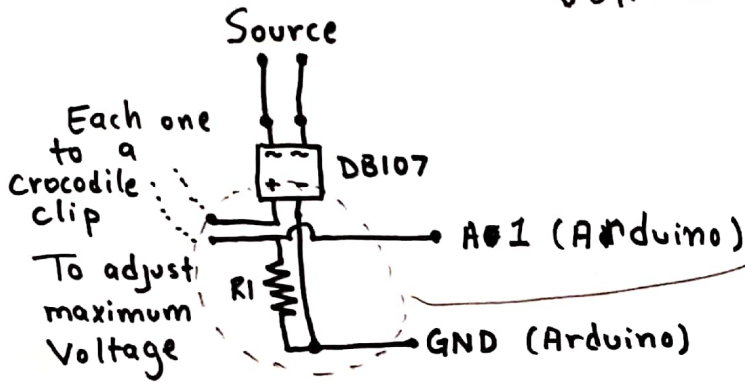

# Ohmmeter circuit

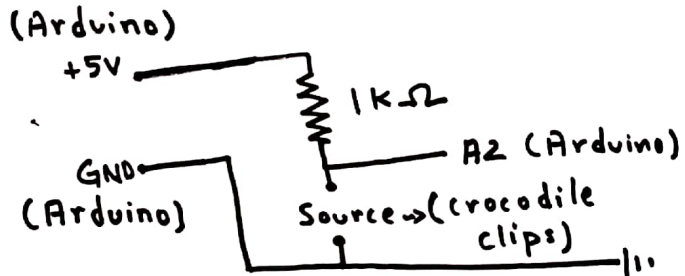

Arduino GND

# Mode change circuit

