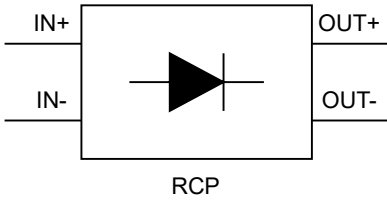
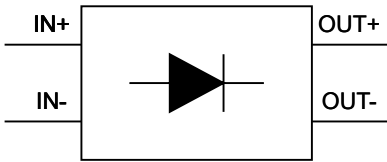


Common reverse current protection solution symbol, used in conversion circuit diagram.



"Ideal Diode" module as reverse current protection. Input and output pad labels may differ in different modules. See the specification and/or datasheet for particular module.



Schottky diode as reverse current protection. Install on V+ rail between voltage source and voltage consumer.

