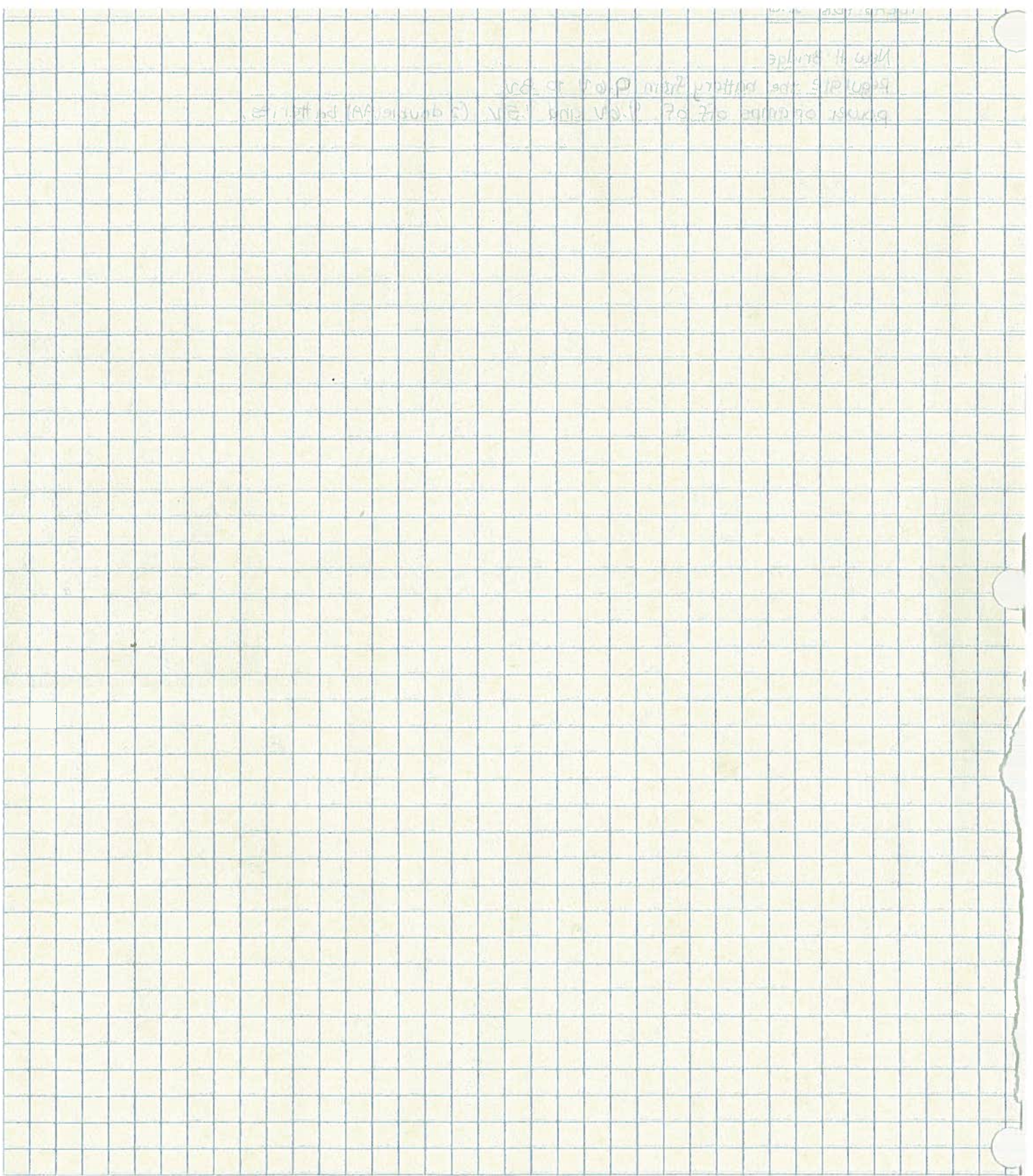


Handwritten text at the top right of the page.

Handwritten text in the upper middle section of the page.




New H-Bridge

Regulate the battery from 9.6V to 8V

power opamps off of 9.6V and 1.5V (2 double(AA) batteries)

Always Tools after use

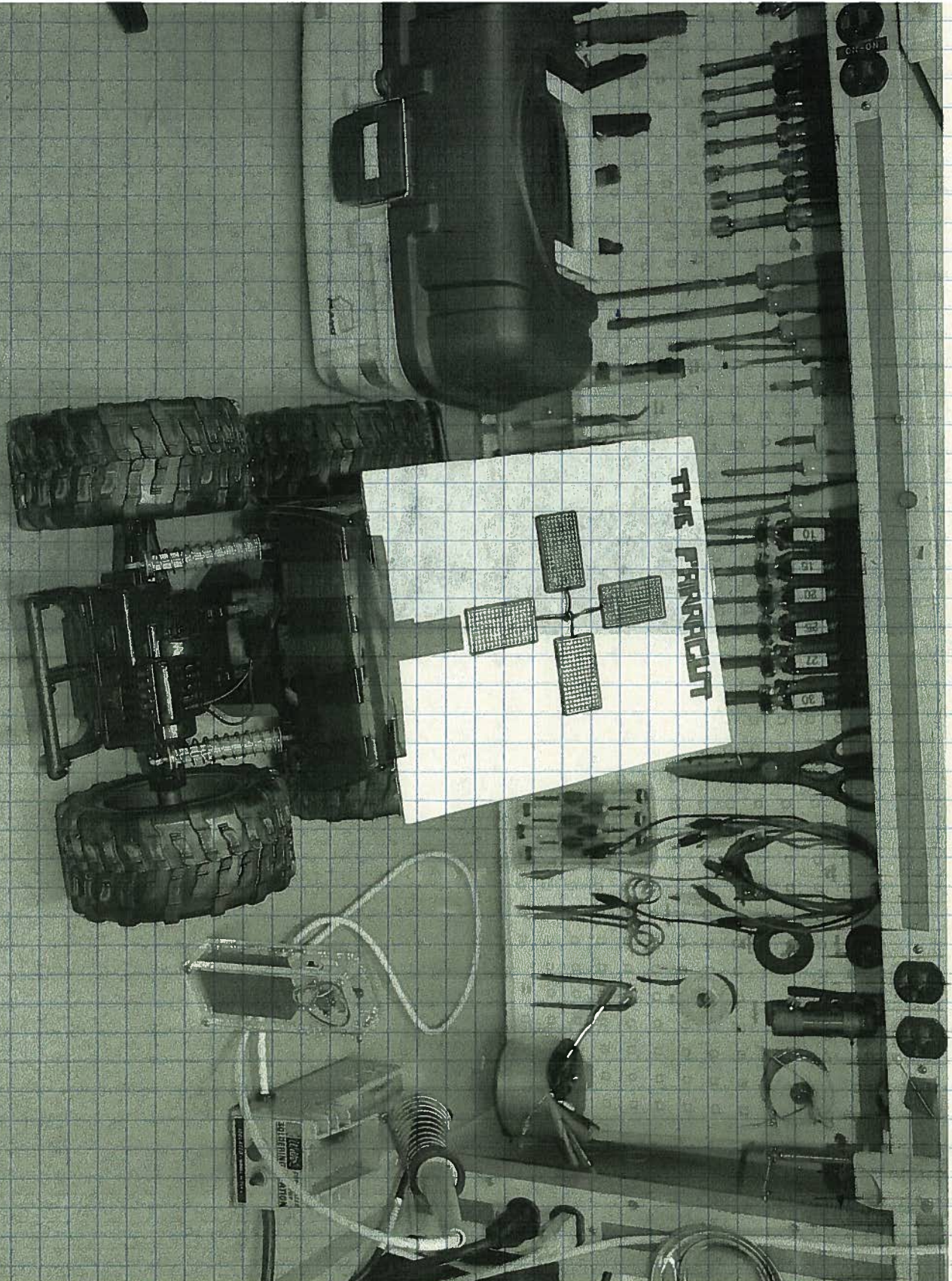

THE CARPENT

WOLFF
ANLUBRIERE
Rapid
100%
WOLFF



TOP


BACK




PICU



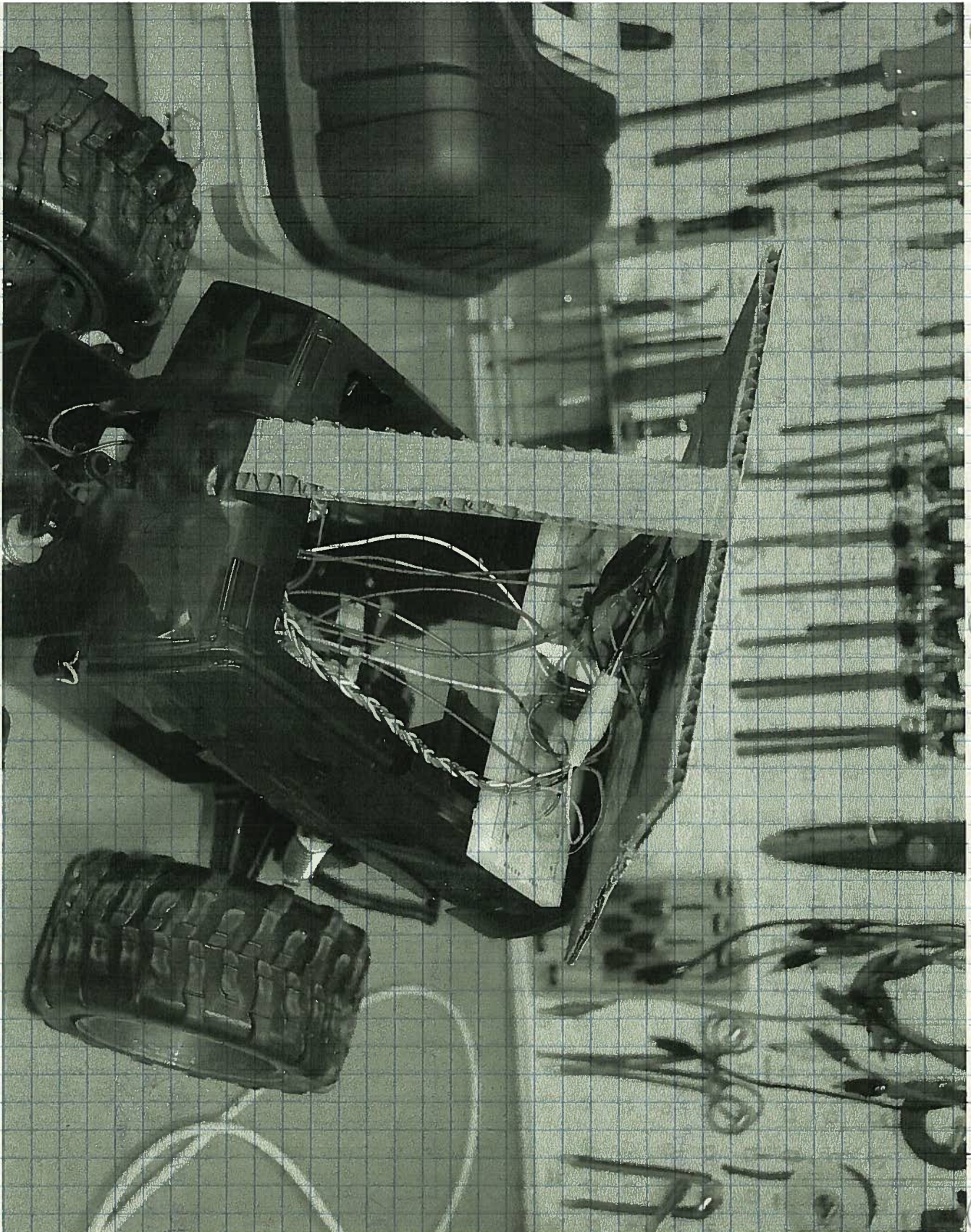
Handwritten notes on graph paper, including the number '25' and some illegible text.



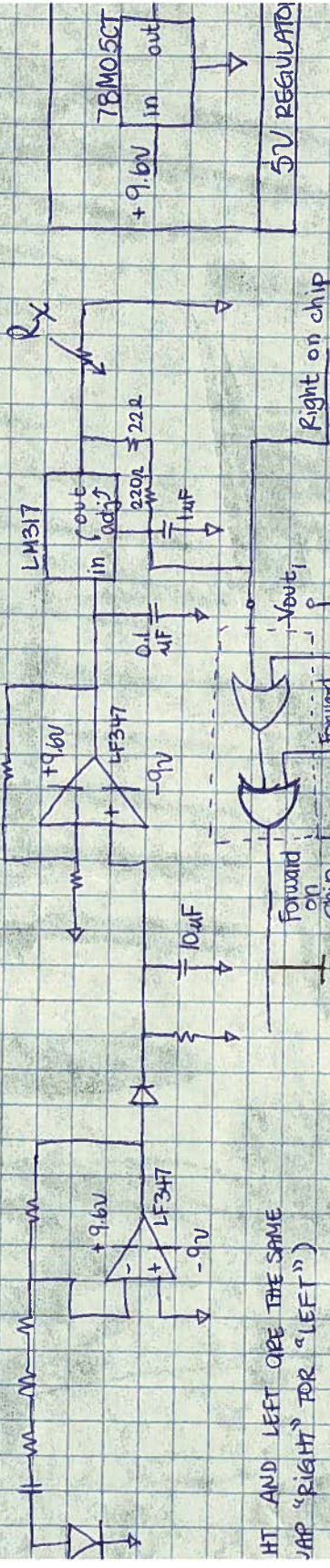

HT AND LEFT ARE THE SAME
VAR "RIGHT" FOR "LEFT"

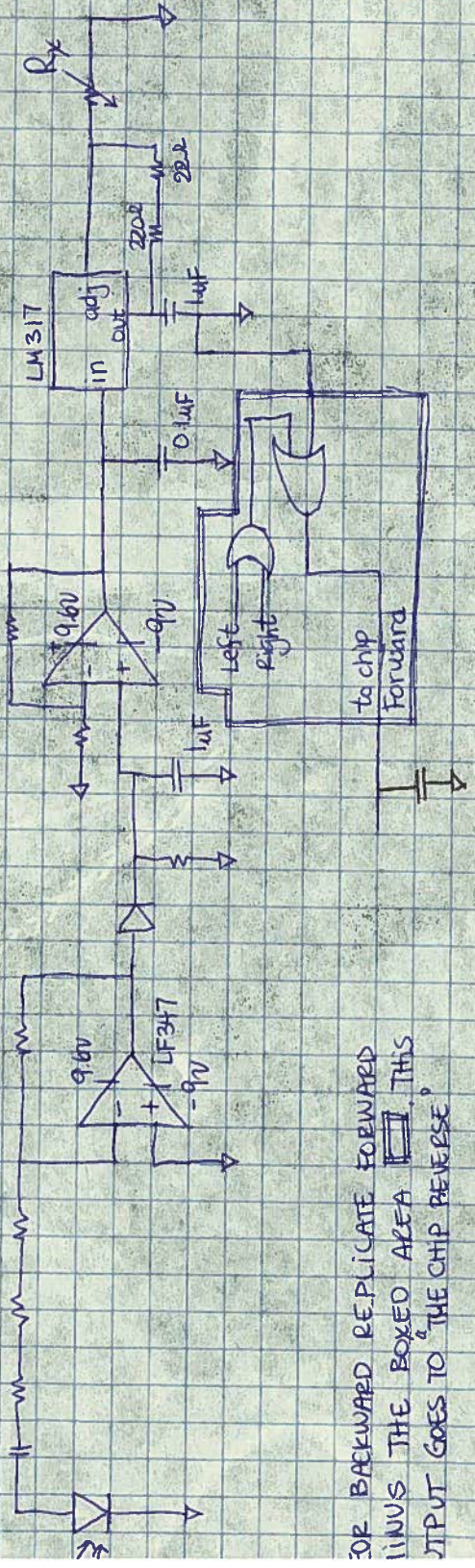
This chip requires 5V to operate
(see 5V REGULATOR)



FOR BACKWARD REPLICATE FORWARD
UNLESS THE BOXED AREA THIS
OUTPUT GOES TO "THE CHIP REVERSE"

R_x needs adjusted to output between $\approx 1.7V$ and $< 3.0V$
if this exceeds $3.0V$ the car will burn out it's in
circuitry.
Consider a capacitor (shown in black $\frac{\square}{\square}$) to fill
any spikes in voltage.

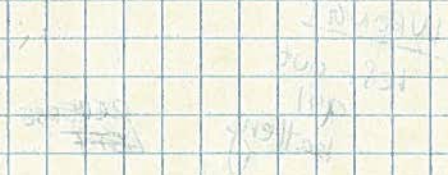To make it sustain right and left (about 2 seconds)



FORWARD AND BACKWARD

Direction	Time (s)	Notes
Right	0.00	
Left	0.00	
Forward	0.00	
Backward	0.00	
Right	0.00	
Left	0.00	
Forward	0.00	
Backward	0.00	
Right	0.00	
Left	0.00	
Forward	0.00	
Backward	0.00	
Right	0.00	
Left	0.00	
Forward	0.00	
Backward	0.00	
Right	0.00	
Left	0.00	
Forward	0.00	
Backward	0.00	

THESE THINGS ARE NOT WORKING AND WE NEED SOME OTHER THINGS TO DO

WRONG!
left out
an
battery

LEFT

FORWARD

~~REVERSE~~

Left	0V
Forward	1.6V
Reverse	0V
Right	0V
Left	3.24V
Forward	0.84V
Reverse	0V
Right	0V
Left	0V
Forward	2.28V
Reverse	0V
Right	0V
Left	0V
Forward	0V
Reverse	1.50V

$2.1 - 1.6 = 0.5$
 $\approx 23\%$

$3.24 - 0.84 = 2.4$
 $\approx 74\%$

VOLTAGES @ OPAMP OUT

(@ Regulator out)

RIGHT	Ri	5.69V	2.0V	THIS TRIGGERS JUST FINE
	L	0.06V	0.0V	
	F	0.03V	1.55V	THIS DOES NOT
	Re	0.0V	0.0V	
LEFT	Ri	0.10V	0.0V	THIS TRIGGERS FINE
	L	0.06V 4.63V	3.13V	
	F	0.03V	0.79V	THIS DOES NOT
	Re	0.01V	0.0V	
REVERSE	Ri	0.10V	0.0V	THIS TRIGGERS JUST FINE
	L	0.05V	0.0V	
	F	0.03V	0.0V	
	Re	6.40V 7.36V	1.50V	
FORWARD	Ri	0.10V	0.0V	THIS TRIGGERS JUST FINE
	L	0.05V	0.0V	
	F	6.71V	2.15V	
	Re	0.0V	0.0V	


THIS SHOWS THAT OUR DIODE SYSTEM DOES NOT WORK CORRECTLY. WE NEED SOME SIMPLE DIGITAL LOGIC


TO DO BOTH FORWARD AND A TURN.

(see voltage tables to right)

THE AFORE MENTIONED SYSTEM OF DIODES FAILS. AFTER RESEARCH IT APPEARS DIGITAL LOGIC IS THE ONLY WAY

LOGIC TREE

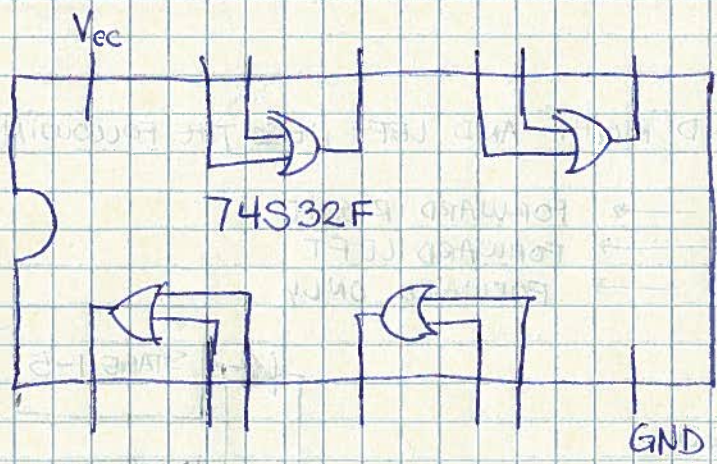

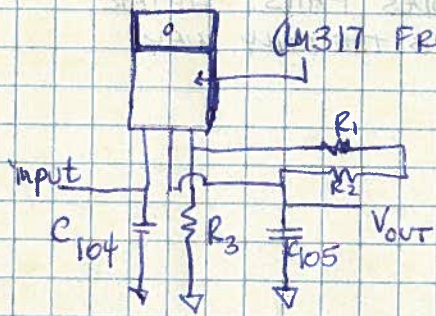

(LM317 FROM T.I)

$$R_1 + R_2 = 242 \Omega$$


R_3 = adjusted to each channel

$$C_{104} = 0.1 \mu F$$

$$C_{105} = 1 \mu F$$

NOTE: THESE ARE GIVEN AS FREE SAMPLES TO PEOPLE WITH VALID REASONS. MINE WAS "STUDENT"

THEREFORE ONE CHANNEL:

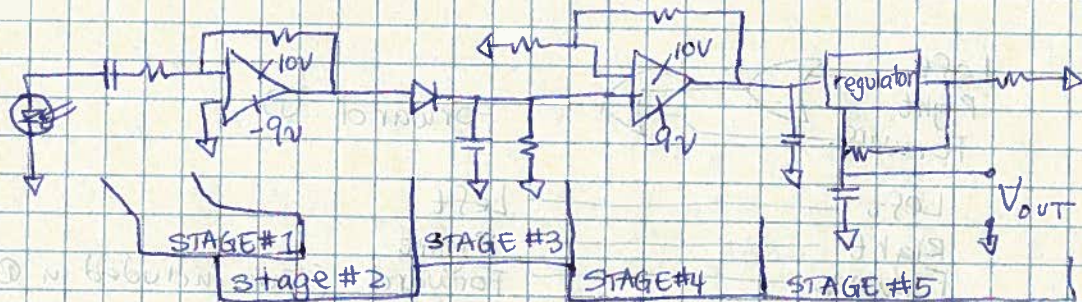


V_{OUT} GOES INTO EACH PIN INTO OUR RC CAR.

PROBLEM:

FORWARD AND RIGHT AND LEFT NEED THE FOLLOWING RELATIONSHIP:

WHEN

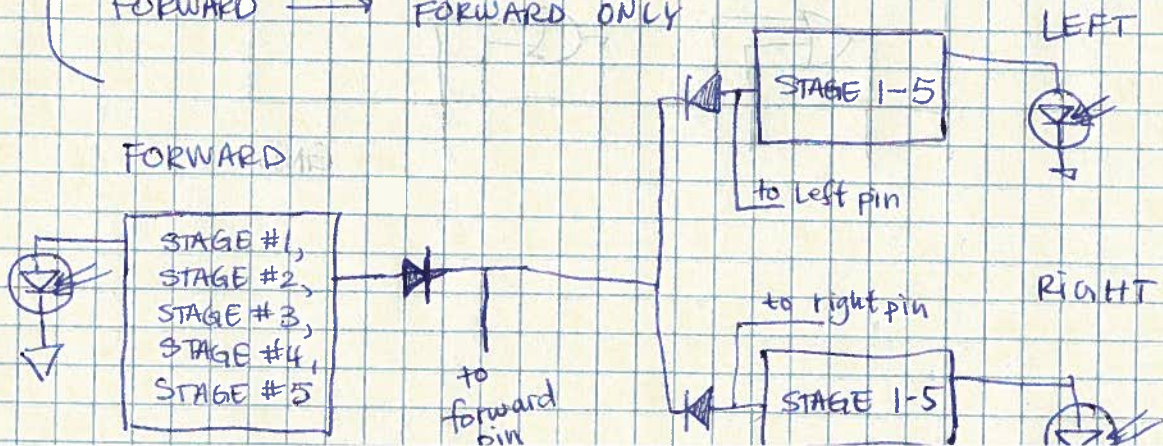- RIGHT → FORWARD RIGHT
- LEFT → FORWARD LEFT
- FORWARD → FORWARD ONLY



DETERMINED FROM SENSOR NEEDS TO NOT LIMITING CONTROLLING OUR TWO STAGES. IS THIS SO?

QUESTION: WHAT ARE THE OPERATING CONDITIONS OF THE RECEIVER?

IE. WHAT RANGE CAN THE SIGNAL BE? 2.5V-3V OR 3V-3.3V?
NEED TO KNOW. SET OUTPUT TO THE MIDDLE OF THIS RANGE OR UPPER 2/3'S, SO WHEN BATTERY DRAINS IT STILL WORKS.

ANSWER: IT APPEARS THAT THE DATASHEET SHOWS

$V_{out} = 2.7V \leftrightarrow 2.7V \leftrightarrow 2.7V$	2.5V	2.8V	3.1V	
$I_{out} = ???$	0.2mA	1.0mA	???	???
MIN	MAX	MAX	MIN	TYP
	TYPICAL			MAX

NO DC-DC CONVERTER


DC-DC CONVERTER

FULL SPEC SHEET @


<http://instructables.com/files/orig/FWN/CD13/GV525G0X/FWWCD13GV525G0X.pdf>

OR SEARCH TX2 RX2 datasheet

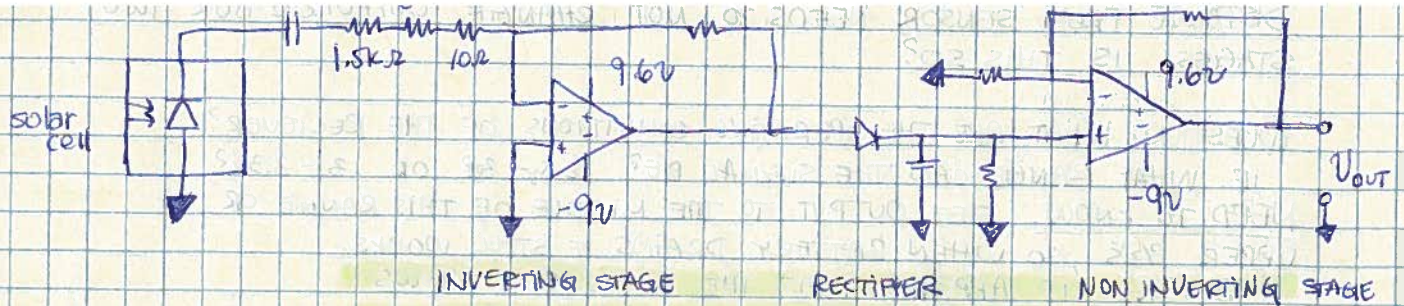
AS IT TURNS OUT, THE LOWER THE VOLTAGES, THE SLOWER THE MOTORS GO. I INTENTIONALLY PUT REVERSE AT ABOUT 1.5V SO IT WAS EASIER TO CONTROL. I AM ALSO CONSIDERING ABOUT 2V ON THE REST TO MAKE STEERING EASIER.



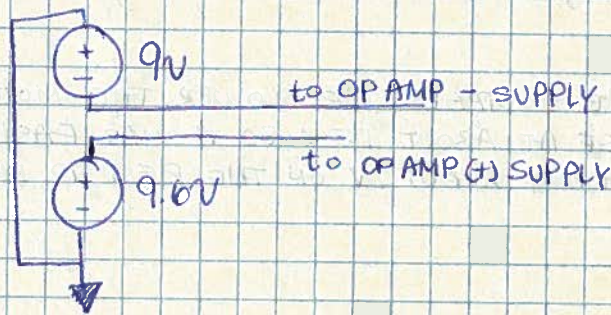
NOTE THAT THE OPAMP HAS TWO DIFFERENT SUPPLYS. THIS IS NOT ACCIDENTAL. THE $-9V$ SUPPLY COMES FROM A 9 VOLT BATTERY, WHERE AS THE $+9.6V$ COMES FROM THE CAR BATTERY ITSELF. THIS WIRING CONFIGURATON IS SHOWN BELOW



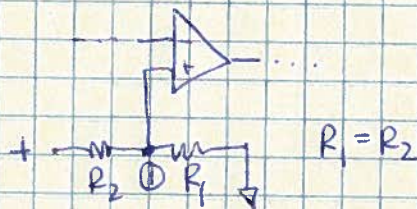THIS IS NECESSARY BECAUSE WE NEEDED TO DECOUPLE THE OUTPUTS OF THE OPAMP. WITH THE SETUP WITH AN ARTIFICIAL GROUND:



WHEN THE SIGNAL WAS ON NONE OF THE CHANNELS, THERE WAS NO PROBLEM. HOWEVER, WHEN A SIGNAL WENT HIGH ON ONE OF THE FOUR CELLS, ALL THE OUTPUTS WENT HIGH. AFTER EXTENSIVE TESTING, I NOTICED THAT UPON TRIGGERING A SIGNAL, THE VOLTAGE AT (1) CHANGED. FOR THIS TO BE A GROUND, THIS CAN NOT HAPPEN. THEREFORE THERE NEEDS BE A CHANGE, OR DECOUPLING, OF THE GROUND. THE ONLY WAY TO DO THIS WAS TO REMOVE THE OPAMP POWER SUPPLY FROM THE MIX OF IT ALL. THUS WE HAVE THE OUTCOME SHOWN.

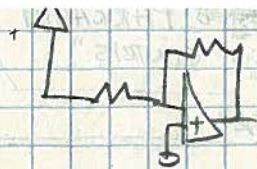

DOES NOT WORK
 CAN'T GET OUR SOLAR CELL TO ACT AS A DIODE.
 UNKNOWN REASON

PARTS LIST

		<u>TOTALS</u>	
✓	4 solar cells	4	4.45
✓	10Ω	4	
✓	82Ω	4	
✓	1.5kΩ	4	
✓	0.01μF	4	
✓	100pF	4	
✓	1μF	4	
✓	1N4148 diode	4	
✓	1kΩ	4	
✓	47kΩ	4	
✓	560kΩ	4	
✓	10kΩ	8	
✓	10kΩ	2	
✓	10kΩ	2	
✓	LF347	2	0.45
	filter x 4		
	stage 2 x 4		
	stage 1 x 4		
	ground stage 2 x 4		
	voltage divider x 2		
	x 2		





$\$0.04 \text{ each} = 32 \times 0.04 = \1.28
 $\$0.1 \text{ each} = 8 \times .1 = \0.80

17.8 (solar)
 0.9 LF347
 0.8
 1.28


 \$ 20.78


THE FOLLOWING MUST BE REPEATED FOUR TIMES TO HAVE.

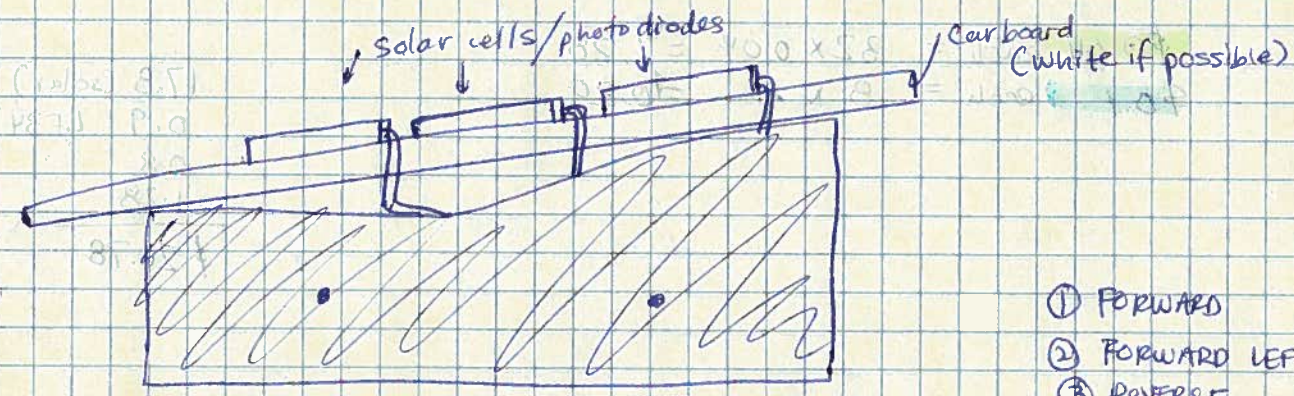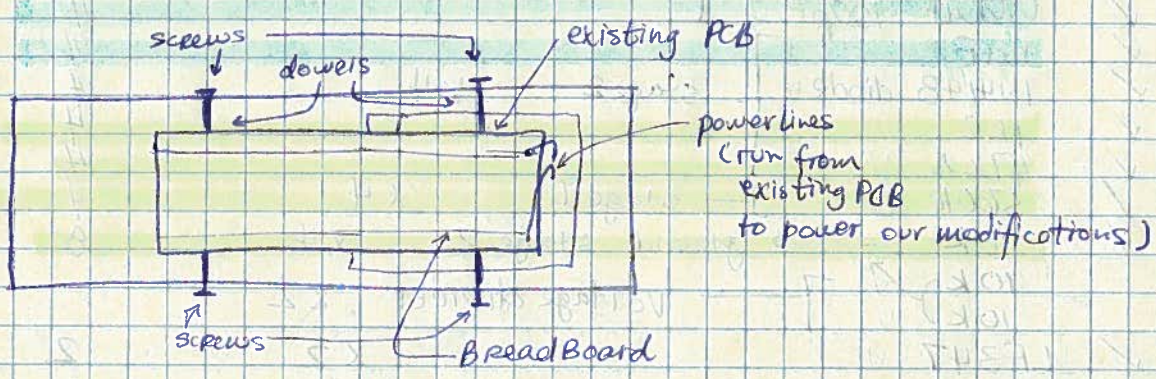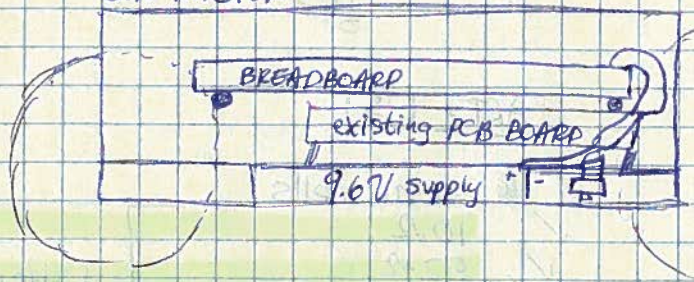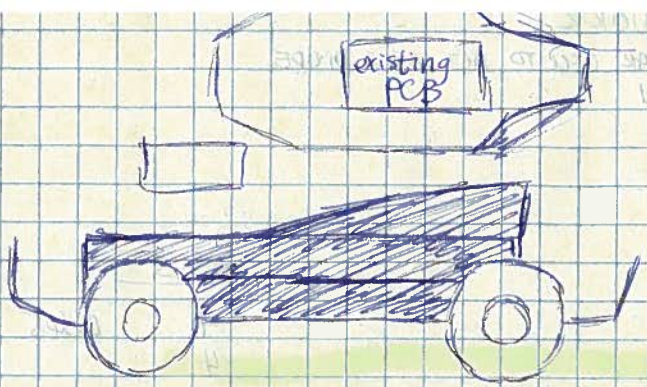
General ~~THURAGUT~~ THURAGUT
 "COPERNICUS CENTRIS"
 "MODEL HZ"
 "SUN RACER"



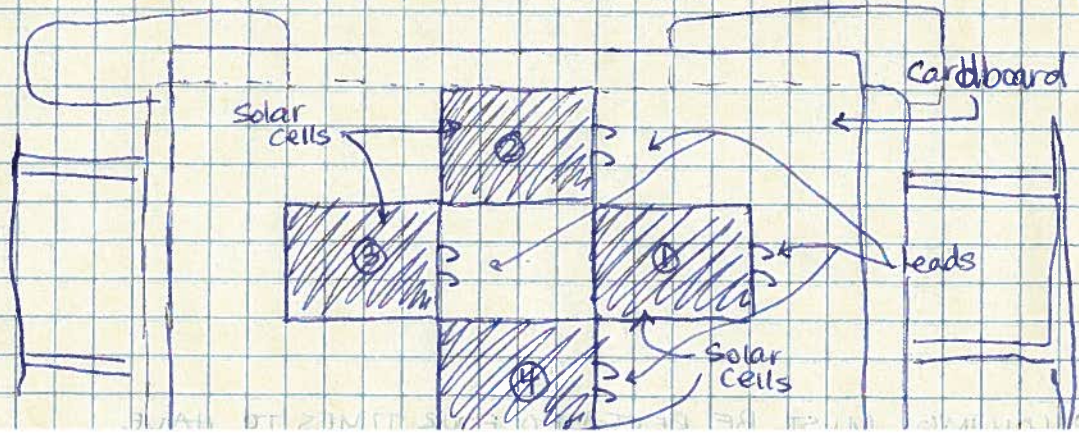- ① FORWARD
- ② FORWARD LEFT
- ③ REVERSE
- ④ FORWARD RIGHT



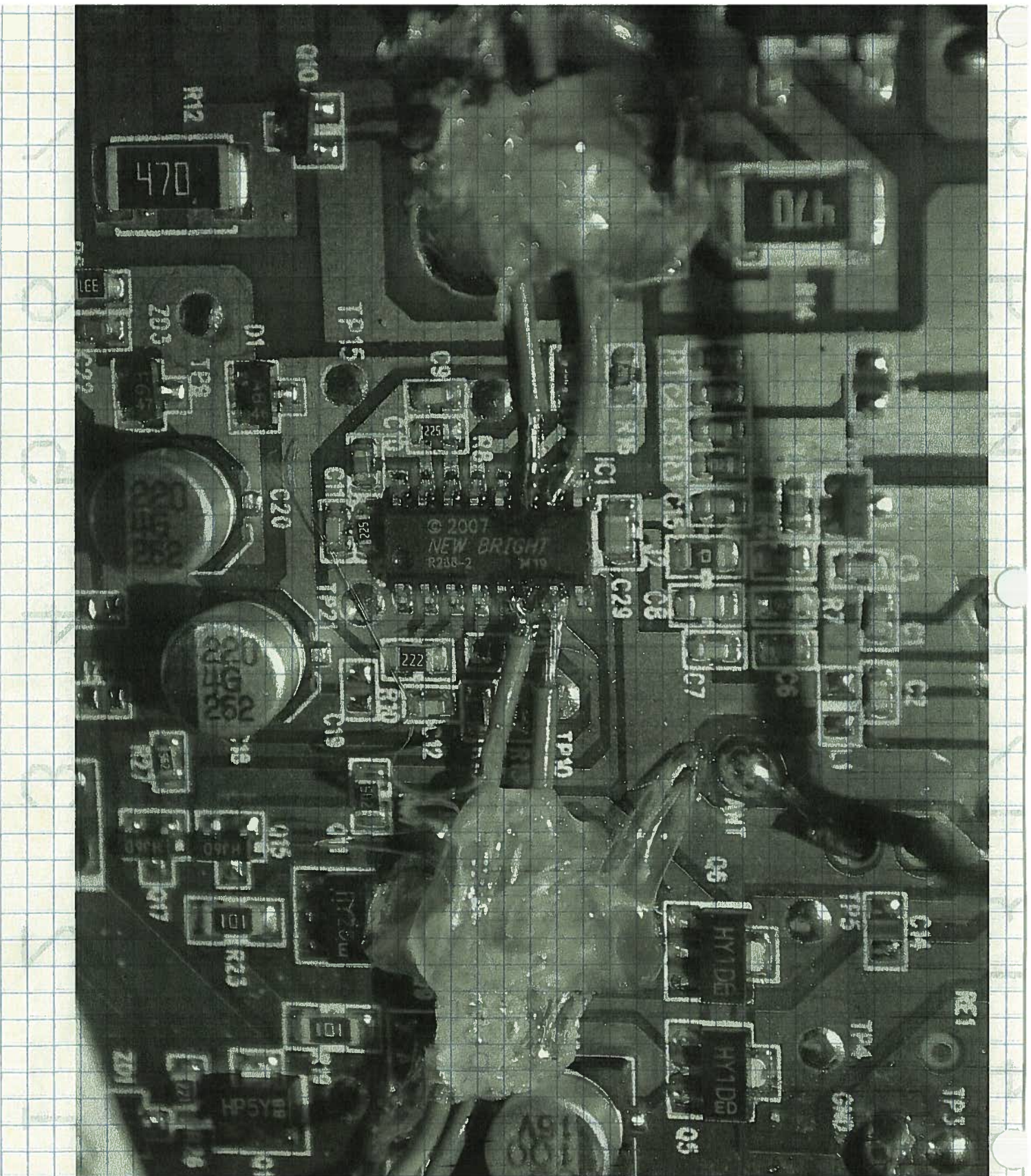

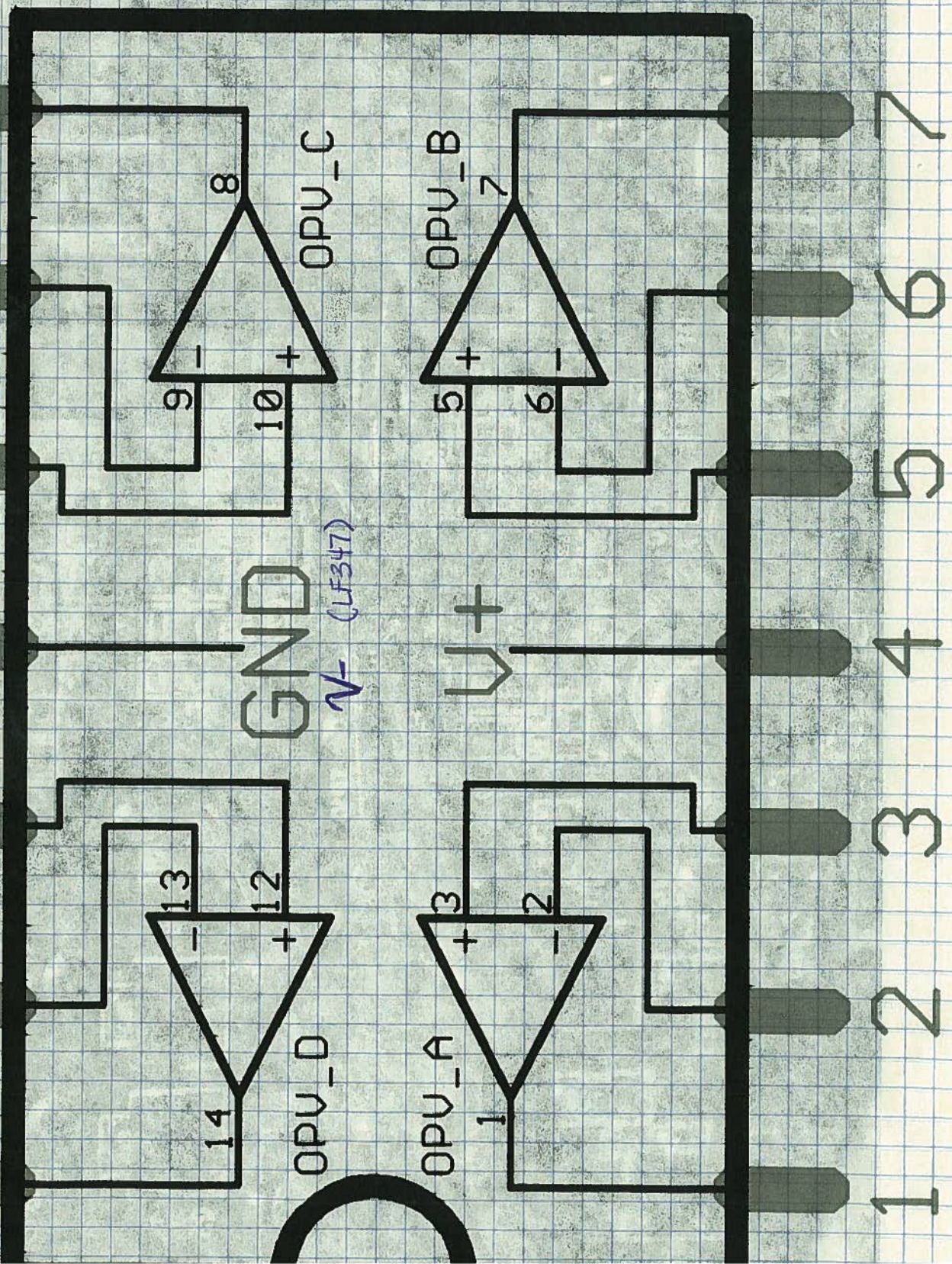

INFRARED $\approx 10^{15}$ 10^{10}

THIS DOES NOT AFFECT OUR CORNER FREQUENCY. I'LL JUST LEAVE IT AS DESIGNED @ 10KHZ.

$$\frac{100}{100} = 1$$

$$180 = 180 + 0$$

$$180 = 180$$

$$180 = 180 + 0$$


$$\frac{180}{180} = 1$$

$$180 = 180 + 0$$

$$180 = 180 + 0$$

$$180 = 180 + 0$$

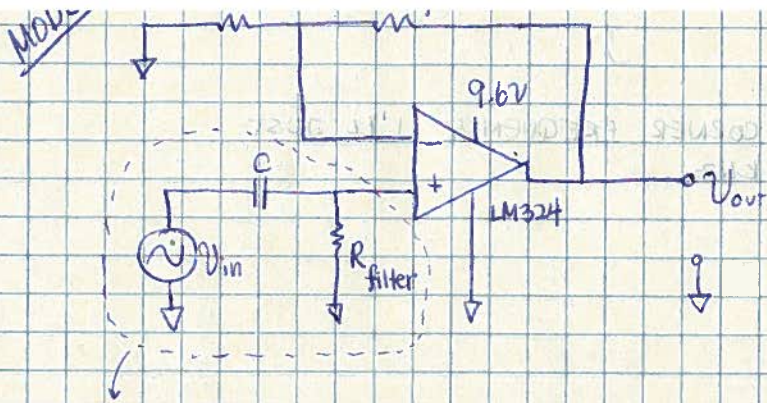NEITHER FEEDBACK NOR CORNER FREQUENCY IS AFFECTED BY THIS



$$A_{MB} = \frac{R_f + R_2}{R_2}$$

(SHOULD BE AS CALCULATED PREVIOUSLY)

THIS IS OUR HIGH PASS FILTER. IT SHOULD HAVE NO PROBLEM B/C IT HAS NO AFFECT ON GAIN. IT SHOULD BE PURLY A FILTER.

WHICH IS CORRECT? MODEL 1 OR MODEL 2 OR BOTH?

PREDICTION: MODEL #2 WILL BE MORE STABLE BECAUSE C IS NOT COUPLED TO OUR OTHER RESISTORS OR OUR OUTPUT.

$$180k = R_f$$

$$184 = \frac{180k + R_2}{R_2}$$

$$\begin{array}{r} 983 \\ - 820 \\ \hline 163 \\ - 150 \\ \hline 13 \end{array}$$

$$184 R_2 = 180k + R_2$$

$$183 R_2 = 180k$$

$$R_2 = 180k / 183 = 983.6 \Omega$$

$$184 = \frac{R_f + 180k}{180k}$$

$$\approx 820 + 150$$

UNUSED

$$180k = R_2$$

$$(184)(180k) = R_f + 180k$$

$$(184)(180k) - 180k = R_f = 32.9 M\Omega$$

$$F = \frac{R_2}{R_2 + R_f} = \frac{970}{970 + 180k} = 0.00536$$

$$f_{H_i} = GBW * F \quad GBW = 1 MHz$$

$$= 1 MHz (0.00536) = 5360 Hz$$

$$712 mV$$

$$1.168 V$$


NEITHER MODEL SEEMS TO WORK. I'M GOING BACK TO TRY THE LF347.

0.010V

$$1592(184-1) = R_f$$


$$(183)(1592) = 292928$$
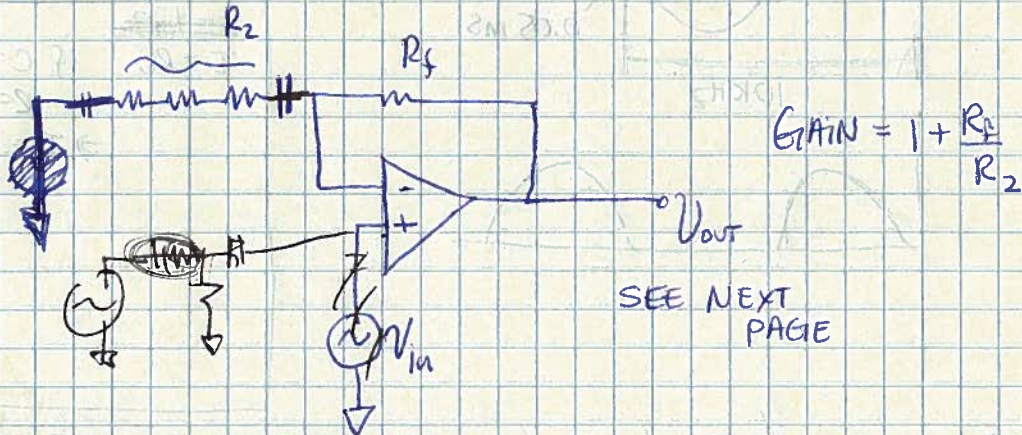
$$= 293 \text{ k}\Omega \approx 270 \text{ k}\Omega + 22 \text{ k}\Omega$$




$$GAIN = 1 + \frac{R_f}{R_2}$$

SEE NEXT PAGE

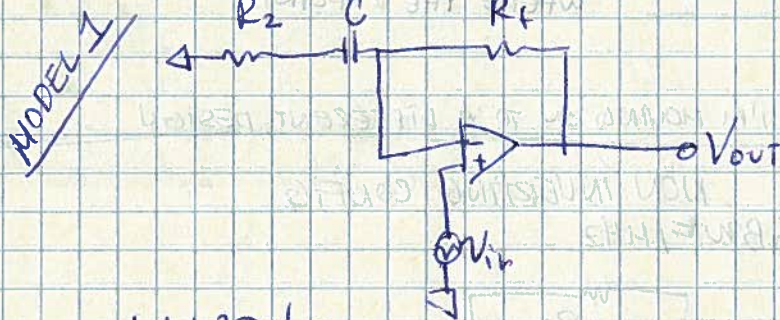


$$Gain = 1 + \frac{292 \text{ k}\Omega}{1592 \Omega}$$

$$= 184 \%$$

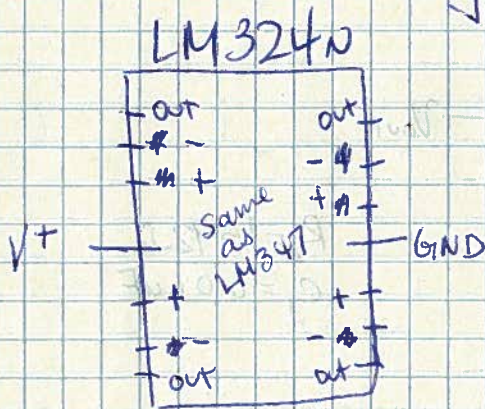

2/8/13

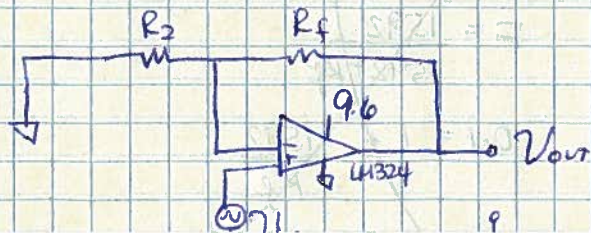As shown above i've not had success with. So i'm going to attempt a simple version of this with just a simple gain, no filters.




$$A_{NB} = R_2 + R_f$$

THEORY



$10\text{kHz} \Rightarrow \frac{1}{10\text{kHz}} = \text{period} = 0.0001\text{ s}$

$V_{in(AC)}$

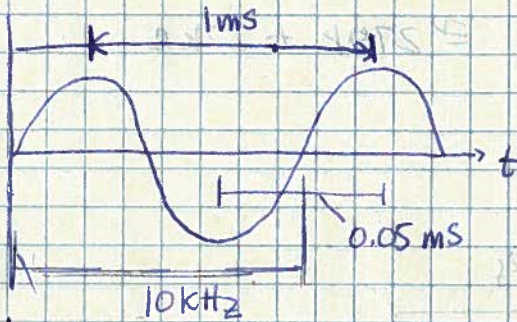

$\tau = RC$ time constant
 $e^{-t/\tau}$ is the decay of
 (↓) on $V_{out(DC)}$

①



~~$\tau = RC$~~ if $C = \text{~~100~~ } 100\mu\text{F}$?
 $R = 1\text{ k}\Omega$?
 $\Rightarrow \tau = 0.1$

$V_{out(DC)}$



THE BIGGER THE C, THE FLATTER THE SLOPES WHERE THE ↓ POINT.

I CAN'T FIX OUR DIODE PROBLEM, SO I'M MOVING ON TO A DIFFERENT DESIGN

LM324N $\$0.74$ 31248


NON INVERTING CONFIG

\hookrightarrow $GBW \approx 1\text{ MHz}$

$F = \frac{R_2}{R_2 + R_f}$ $A_{MB} = \frac{R_2 + R_f}{R_2}$

$f_H = GBW * F$

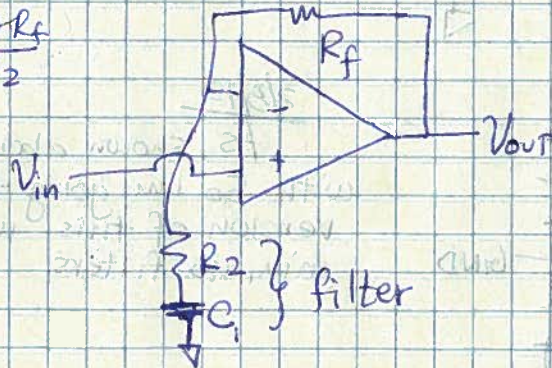$\frac{10\text{kHz}}{1\text{MHz}} = F$
 $0.1 = F$



$R_2 = 1592\Omega$
 $C_1 = 0.01\mu\text{F}$

~~$F = \frac{1592}{1592 + R_f}$~~
 ~~$0.1 = 1 + \frac{1592}{R_f}$~~

~~$A_{MB} = \frac{1592 + 1709}{1592}$~~

$A_{MB} = \frac{1592}{R_f} + 1$

4. MY51451366, Fri Feb 01 04:12:45 2013


2 100W

0.6s

50.00%

Auto

2 26.2V

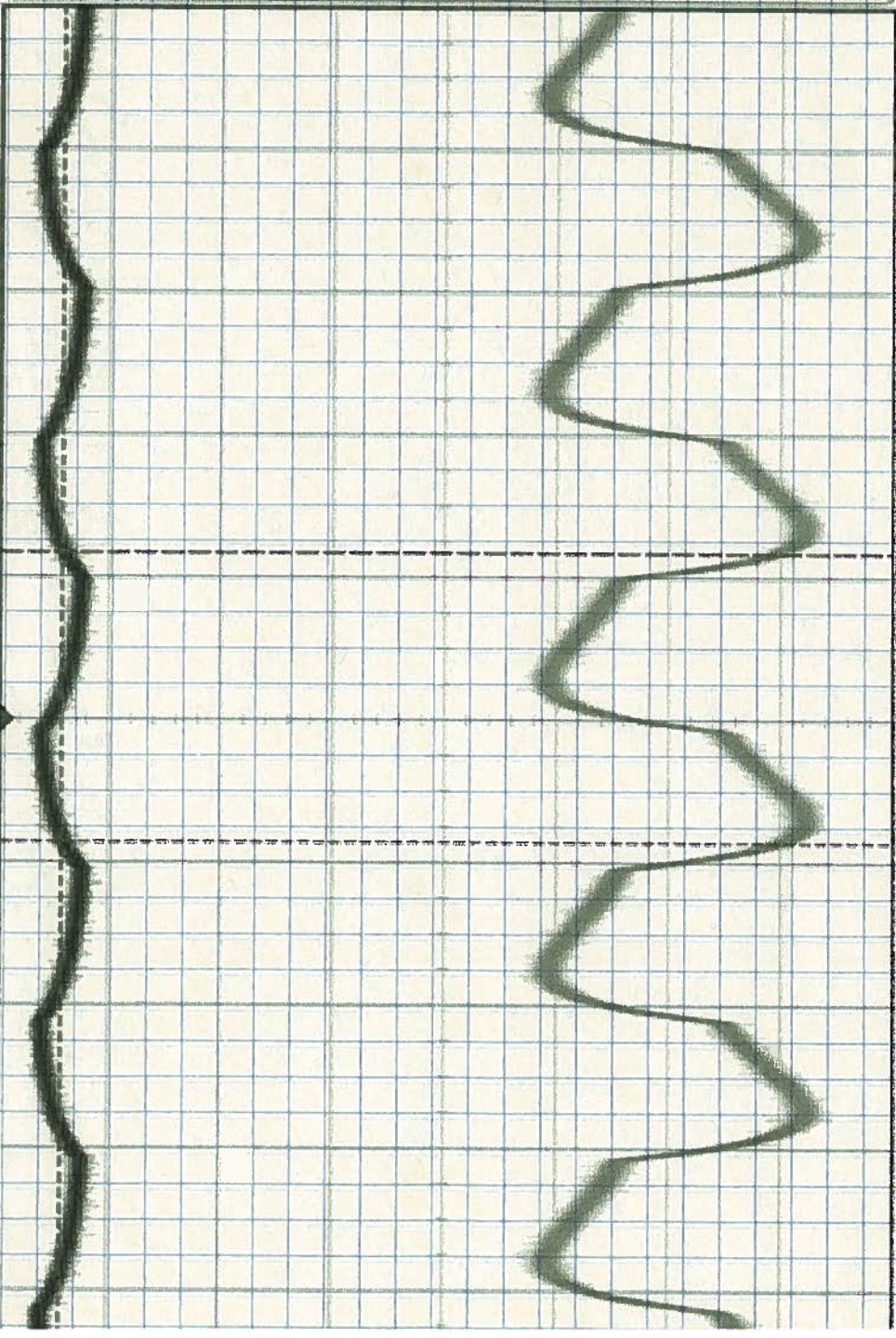

Agilent

Acquisition
Normal
50.0MSa/s

Channels
DC 10
DC 10

Measurements
Pk-Pk(1): 56mV

Pk-Pk(2): 273mHz

Freq(2): 9.816kHz

Freq(1): 9.785kHz

er Menu

to go
PCAD


Load
File

Delete
File

Scope_2.bmp

quadr. 1 score

MSM 19

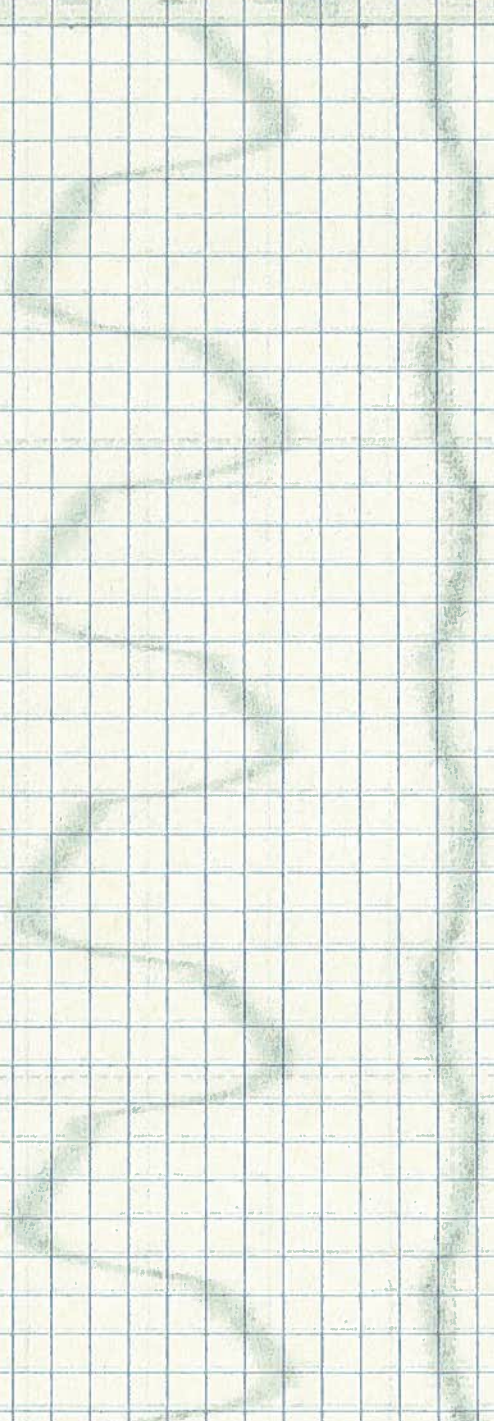


2 100V/

0.0s 50.00ns/

Auto

f 2 26.2V

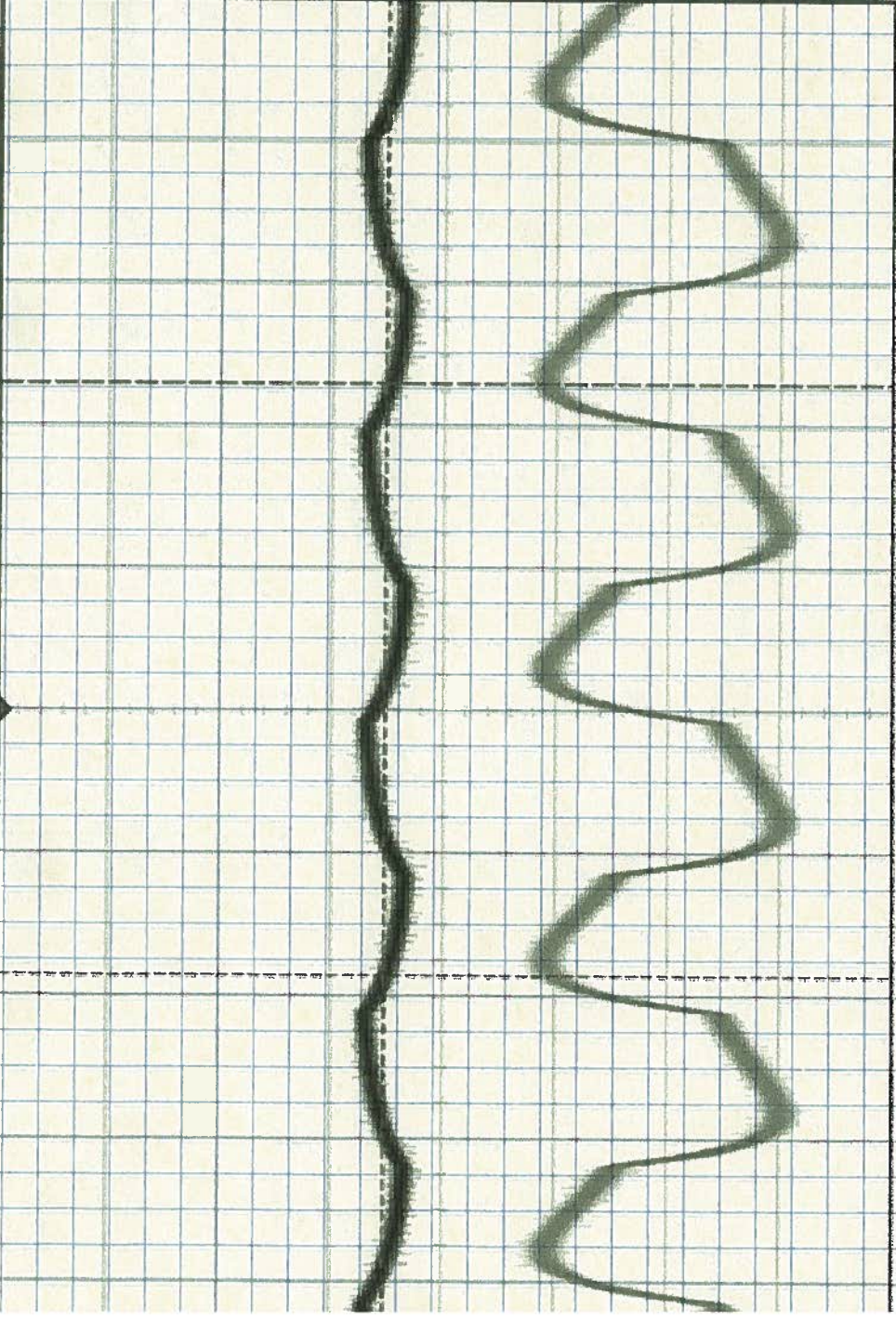

Acquisition	
Normal	
50.0MSa/s	

Channels	
DC	10.0
DC	10.0

Measurements	
Pk-Pk(1):	56V

Pk-Pk(2):	241m
-----------	------

Freq(2):	9.804kHz
----------	----------

Freq(1):	4.8174kHz
----------	-----------

ar Menu

to go

Load File

Delete File

Scope-1.bmp

2 100V/

0.0s


50:00s/

Auto

5

2

26:29

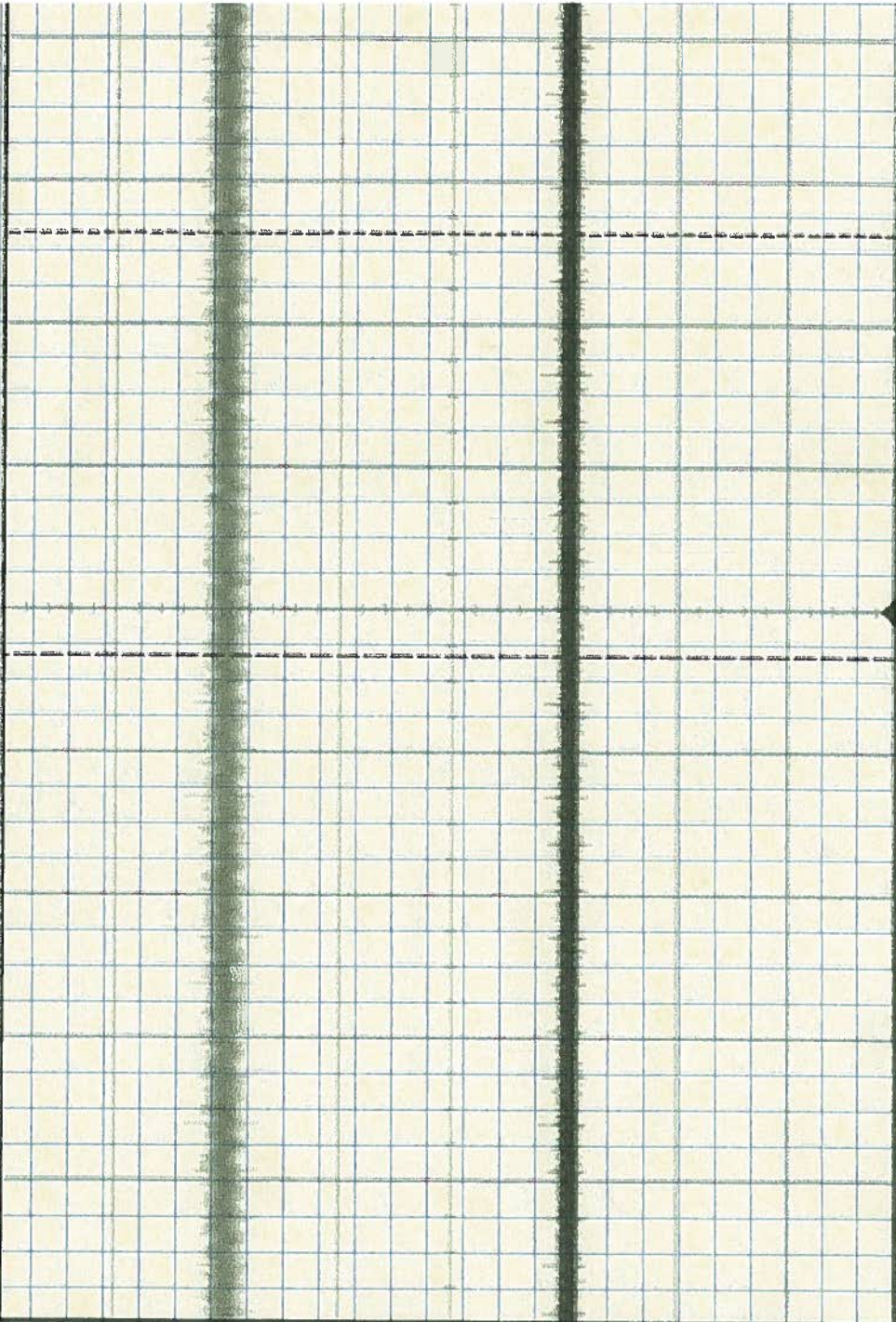

er Menu

to go PCAD

Load File Delete File

Agilent

Acquisition
Normal
50.0MSa/s

#	Channels
DC	101
DG	101

Measurements	Value
Pk-Pk(1):	360
Pk-Pk(2):	480
Freq(2):	105.3kHz
Freq(1):	6.750kHz

Scope - 0. bmp

1901

200

100

100

100

100

100

100

100

100

100

100

100

100

100

100

100

100

100

100

1901

100



$$(244.5 \times 1592) = K_f$$

$$389244 = R_f$$

$$\approx 400 \text{ k}\Omega$$


STANDARD VALUE RESISTORS

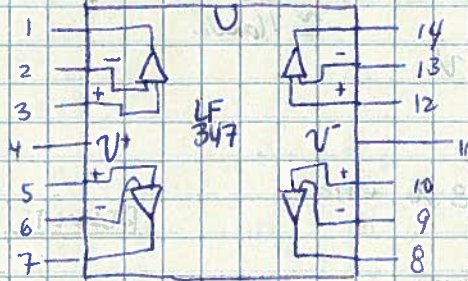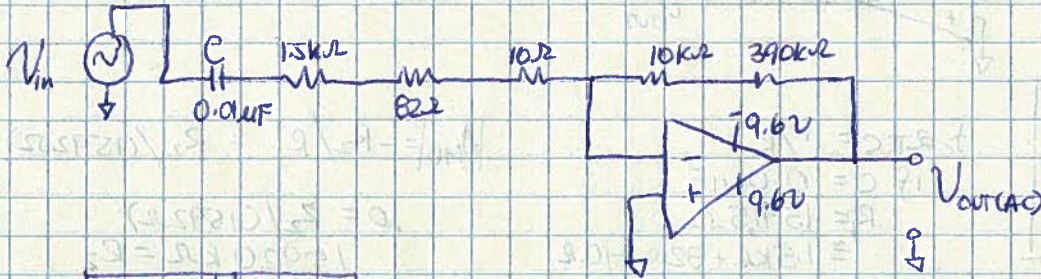- ① $390 \text{ k}\Omega + 10 \text{ k}\Omega = 400 \text{ k}\Omega$
- ② $470 \text{ k}\Omega = 470 \text{ k}\Omega$



NOTE

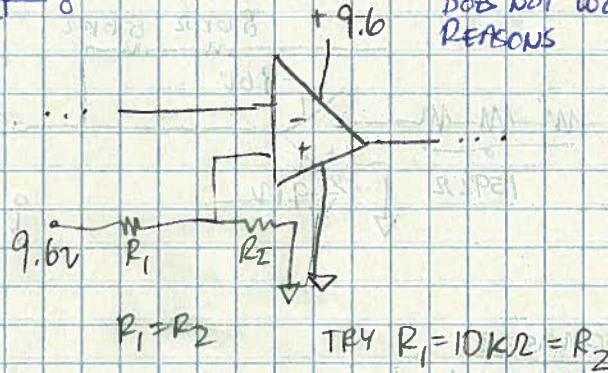
THIS PORTION WORKS VERY WELL, EVEN WITH THE SOLAR CELL (A NON PERFECT SOURCE). BUT WHEN COUPLED WITH THE DIODE IT DOES NOT WORK WELL, FOR UNKNOWN REASONS



NOTE:


THIS SET UP BECAUSE BATTERY AS NO (-) IS LABELED (-)

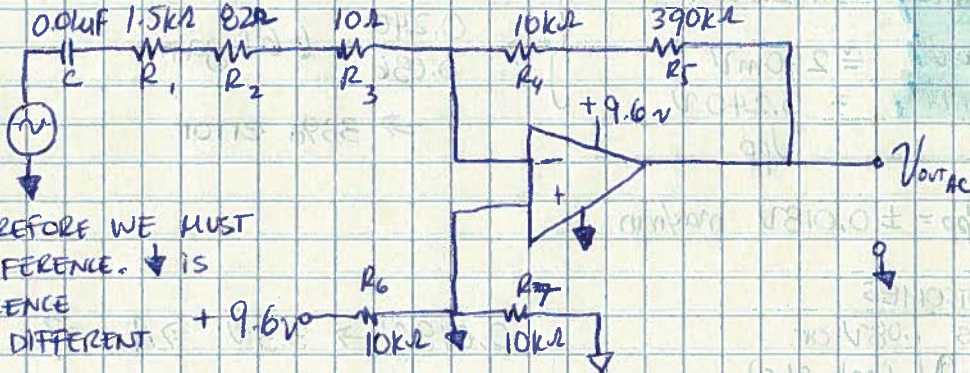A GROUND. THEREFORE WE MUST CREATE A NEW REFERENCE. \downarrow IS THAT NEW REFERENCE POINT (WHICH IS DIFFERENT FROM \downarrow)



still w/ resistors @ gain for 10%, but with only (+9.6V perfect source)
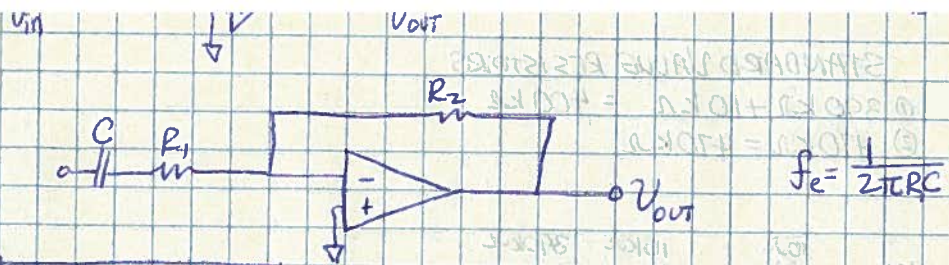
$$\frac{4.2 \text{ V}}{460 \text{ mV}} = 9.13 \text{ } \frac{\text{V}}{\text{V}} \text{ gain}$$



$$f_c = \frac{1}{2\pi RC}$$

DESIRED OUTCOMES
 $f_c \approx 10 \text{ kHz}$
 $A_{MB} \approx 10\%$

$$f_c 2\pi C = 1/R_1$$

if $C = 0.01 \mu\text{F}$
 $R_1 = 1591.5 \Omega$
 $\approx 1.5 \text{ k}\Omega + 82 \Omega + 10 \Omega$

$$|A_{MB}| = -R_2/R_1 = R_2/(1592 \Omega)$$

$$10 = R_2/(1592 \Omega)$$


$$15.920 \text{ k}\Omega = R_2$$

$$\approx 16 \text{ k}\Omega$$

470 mV \rightarrow Gain 10% \rightarrow 0.47V expected = 4.7V
 3.3V = measured

$$\frac{4.7 - 3.3}{3.3} = 42\% \text{ error}$$
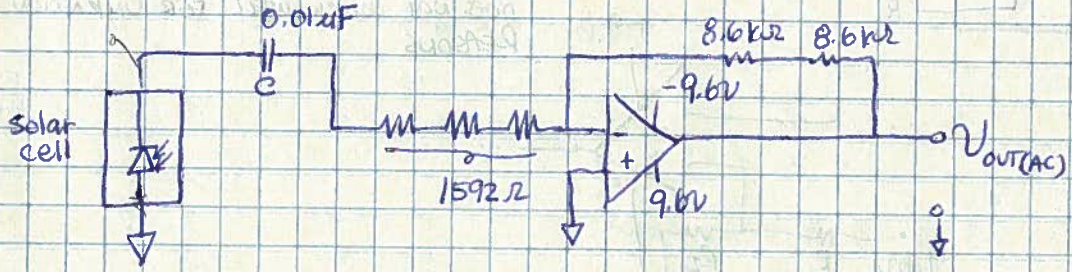
$$\frac{3.3 - 4.7}{4.7} = 29.78\% \text{ error}$$



RESULTS
 SCOPE_0.bmp \rightarrow ambient Light
 SCOPE_1.bmp \rightarrow signal
 (-) input
 (+) ground
 SCOPE_2 \rightarrow signal
 (+) input
 (-) ground

OUTPUT W/MODULATED LASER

BEFORE GAIN	AFTER GAIN
$\approx 0.036 \text{ V}$	$\approx 240 \text{ mV}$
$= 36 \text{ mV}$	$= 0.240 \text{ V}$
V_{pp}	V_{pp}

$$\left. \begin{array}{l} \\ \\ \end{array} \right\} \Rightarrow \frac{0.240}{0.036} = 6.67 \text{ gain}$$

$$\Rightarrow 33\% \text{ error}$$

$$0.036 \text{ V}_{pp} = \pm 0.018 \text{ V max/min}$$

DESIRED OUTCOMES


A_{MB} makes 1.08V or greater on V (not V_{pp}) for micro controller
 OR

3.3V $V_{out(AC)}$ NOT V_{pp} w/out micro controller.

$$0.018 \text{ V} \rightarrow 3.3 \text{ V} \Rightarrow A_{MB} = ?$$

$$\frac{3.3 \text{ V}}{0.018 \text{ V}} = 183.33\% = A_{MB} \text{ GAIN}$$
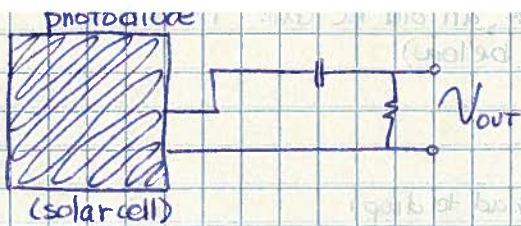
$$\frac{6.6 \text{ V}}{0.036 \text{ V}} = 183.33\% = A_{MB} \text{ GAIN}$$



$$f_c = \frac{1}{2\pi RC} \quad \tau = RC$$

desired 10kHz = $1/2\pi RC$
 $f_c = 10\text{kHz}$

$$\pi = 3.14159265358979$$

$$(2\pi)(10\text{kHz}) = \frac{1}{RC}$$


$$(2\pi)(10\text{kHz})C = 1/R$$

C = 100 μ F	①	0.15195	= R
10 μ F	②	1.5195	
1 μ F	③	15.915	
0.1 μ F	④	159.15	
0.01 μ F	⑤	1591.5	
0.001 μ F	⑥	15915.0	
100 pF	⑦	159150.0	

① & ② & ③ are too small to work with (with respect to R)

STANDARD RESISTOR VALUES

a) 15 + 1.0 = 16 Ω	error (%)
b) 150 + 9.1 = 159.1 Ω	0.53 %
c) 1.5k + 91 = 1591.0 Ω	0.06 %
d) 15k + 910 = 15910 Ω	0.009 %
e) 150k + 9.1k + 051 = 159151 Ω	0.03 %
	0.0006 %

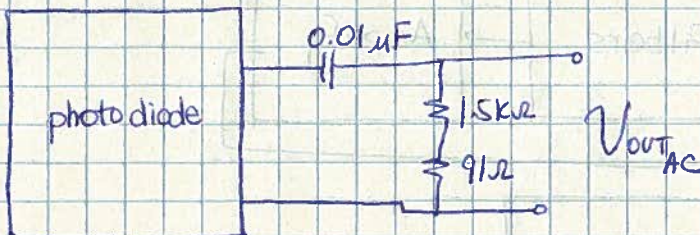


10 KHz modulated laser drives a truck, an old RC car. There are several ideas for approaching this. (see below)

CONSTRAINTS


- \$25 max spending limit
- no new motors
- no new power sources (this one I had to drop)

Idea ① "All Analog" / "Solar cell Method"

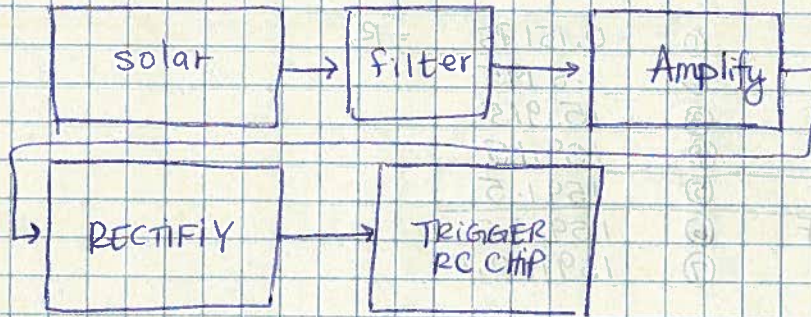USE 4 solar cells, filter out unwanted AC signals and use this to trigger to existing circuit of the RC car.



IDEA ② "Image processing"

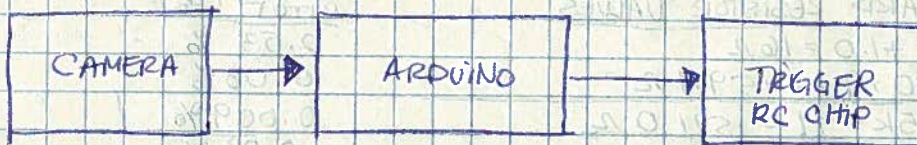

IDEA ③ "Modulation Method"

