



For 60v @12mA

For 60v @12mA

$$\text{Reactance } (X_c) = \frac{311 \cdot 60}{0.12} = 2091 \text{ Ohms}$$

$$\text{Capacitance } (C_s) = \frac{1}{2} \cdot 3.14 \cdot 50 \cdot 2091 = 1.5 \mu\text{F}$$

TITLE: Sheet_1		REV: 1.0
	Company: Your Company	Sheet: 1/1
	Date: 2023-05-20	Drawn By: sagar saini