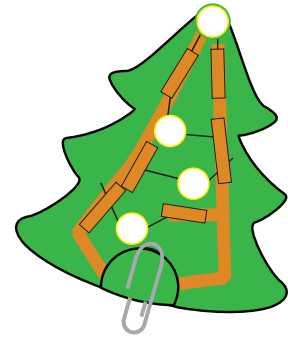



Paper Craft Christmas Tree!



YOU WILL NEED:

TIME:

5-10 MINUTES

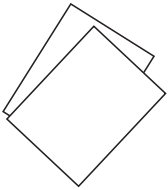


Paper
(Colorful
Construction Paper
or Card Stock.)




Scissors



**Conductive
Tape**

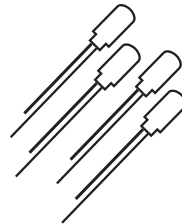

**4
LEDs**

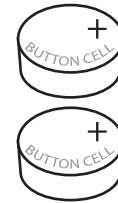


**2
Batteries**



**1 Paper
Clip**

1 CUT OUT PAPER SHAPE
Use template page to help if needed.

2 FOLD BOTTOM

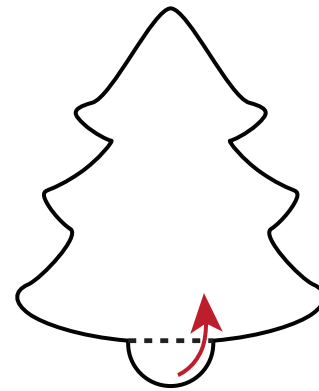

3 APPLY CONDUCTIVE TAPE
Apply lines of tape as shown.




4 **APPLY LEDs onto TREE**

Bend LED legs.

The long LED legs go on the left side of the tree.


The short LED legs go on the right side of the tree.

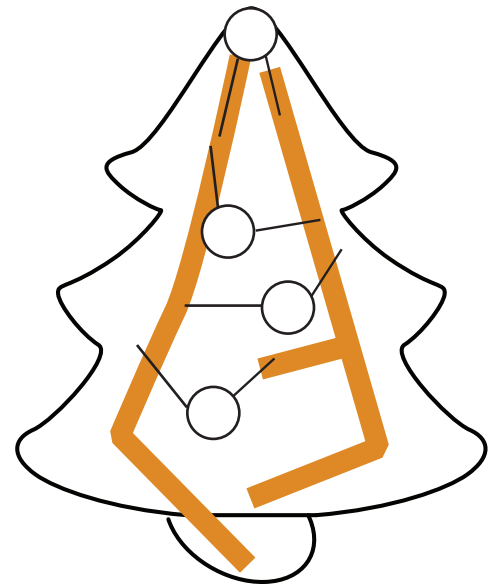Stick them down with more conductive tape.



5 **STACK 2 BATTERIES**

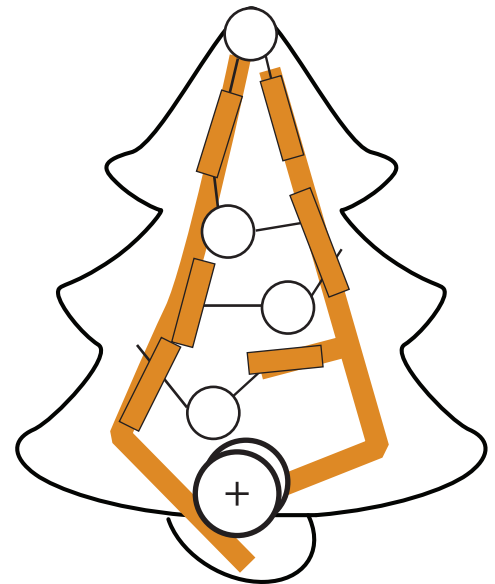near bottom of fold. The positive side of both batteries marked "+" must face up.



6 **PAPERCLIP the BATTERIES**


Position paperclip vertically so that it holds batteries between fold of paper.

Your tree should light up!

If not, check~

- If **none** of the LEDs light up, flip the batteries and try again.
- If **one** of the LEDs does not light, one of two things could be the problem:

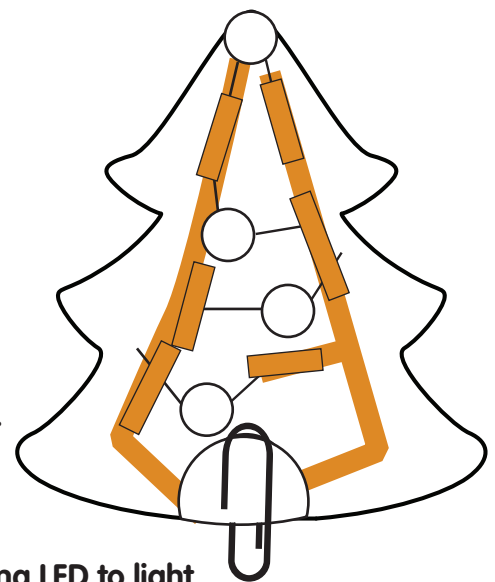- ① The copper tape is not secure around the LED legs.
Press around them and see if you can get the offending LED to light.
- ② One of your LEDs is backwards.
Gently peel the tape off the LED legs and switch it around.



Please visit www.BrownDogGadgets.com for more great ideas & info.

USE THIS TEMPLATE

to help with the shape of your Christmas tree. (You can fit a couple trees on a sheet.)

