

Name! That! Gate!

Logic Gate Characteristics

2-Input AND			
c	b	a	Y
	0	0	0
	0	1	0
	1	0	0
	1	1	1

2-Input OR			
c	b	a	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	1

3-Input AND			
c	b	a	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

3-Input OR			
c	b	a	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

2-Input NAND			
c	b	a	Y
	0	0	1
	0	1	1
	1	0	1
	1	1	0

2-Input NOR			
c	b	a	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	0

3-Input NAND			
c	b	a	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

3-Input NOR			
c	b	a	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

2-Input XOR			
c	b	a	Y
	0	0	0
	0	1	1
	1	0	1
	1	1	0

2-Input XNOR			
c	b	a	Y
	0	0	1
	0	1	0
	1	0	0
	1	1	1