Garage Door Alarm and Auto-Closer
in a Photo Frame
(with Wireless Communication)

https://github.com/slaout/garage-door-alarm-auto-closer

Dashboard (house-side)

100Ω

10µF

0.1µF

100Ω 100Ω 2kΩ 330Ω 1kΩ

Controller (garade-side)

10µF

0.1µF

100Ω 1kΩ

47µF

Garage Door

V-153-1C25

V-153-1C25

Garage
Door
Motor